

# **Computer Logic and Digital Circuit Design (PHYS306/COSC330): Unit 2**

---

Jordan Hanson

October 12, 2021

Whittier College Department of Physics and Astronomy

## Summary

---

# Unit 2 Summary

## Functions of Combinatorial Logic

**Reading:** 6-1 - 6-6 (Tuesday)


**Reading:** 6-7 - 6-11 (Thursday)

1. Half-Adders and Full-Adders
  - Example from study guide
  - Propagation delays
2. Comparators
  - The XNOR gate
  - Multi-bit comparators
  - Inequalities
3. Decoders/Encoders
  - Binary to decimal circuits
  - Decimal to binary circuits
4. Multiplexing and Demultiplexing

## **Half-Adders and Full-Adders, Ripple-Carry**

---

# Half-Adders and Full-Adders, Ripple-Carry

 

**Figure 1:** The desired inputs and outputs of the half-adder. There is no carry-input.

# Half-Adders and Full-Adders, Ripple-Carry

**TABLE 6-1**

Half-adder truth table.

<i>A</i>	<i>B</i>	$C_{\text{out}}$	$\Sigma$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


$\Sigma$  = sum

$C_{\text{out}}$  = output carry

*A* and *B* = input variables (operands)


**Figure 2:** The truth table of the half-adder for 2-bits. What gate action does this match?

## Half-Adders and Full-Adders, Ripple-Carry

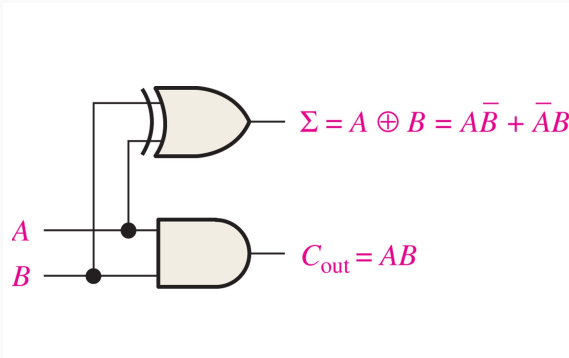

**Figure 3:** The logic function circuit diagram for the half-adder.

# Half-Adders and Full-Adders, Ripple-Carry

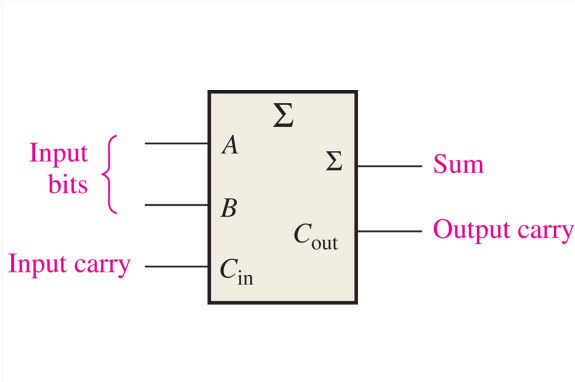

**Figure 4:** The desired inputs and outputs for the full-adder, with carry-input and carry-output.



# Half-Adders and Full-Adders, Ripple-Carry

**TABLE 6-2**

Full-adder truth table.

$A$	$B$	$C_{in}$	$C_{out}$	$\Sigma$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$C_{in}$  = input carry, sometimes designated as  $CI$


$C_{out}$  = output carry, sometimes designated as  $CO$

$\Sigma$  = sum


$A$  and  $B$  = input variables (operands)

**Figure 5:** The truth table for the full-adder is more complex due to the increased number of inputs.
 
# Half-Adders and Full-Adders, Ripple-Carry



 
(a) Logic required to form the sum of three bits



(b) Complete logic circuit for a full-adder (each half-adder is enclosed by a shaded area)


**Figure 6:** Circuit diagrams for the half-adder (left) and full-adder (right).

# Half-Adders and Full-Adders, Ripple-Carry

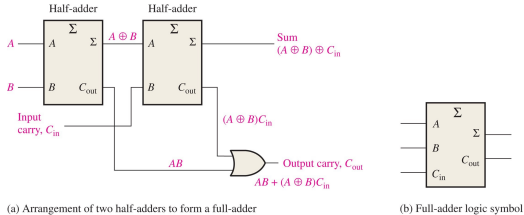


**Figure 7:** Two half-adders to form a full-adder.

# Half-Adders and Full-Adders, Ripple-Carry

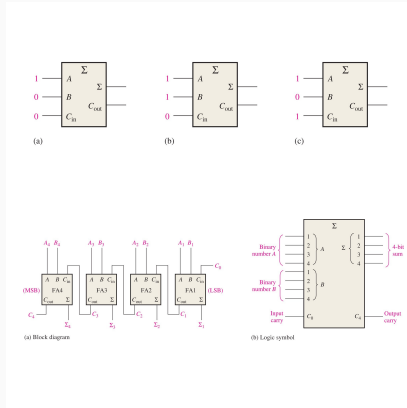


**Figure 8:** Four FA (full-adders) to add bits to the numbers being added.

## Half-Adders and Full-Adders, Ripple-Carry

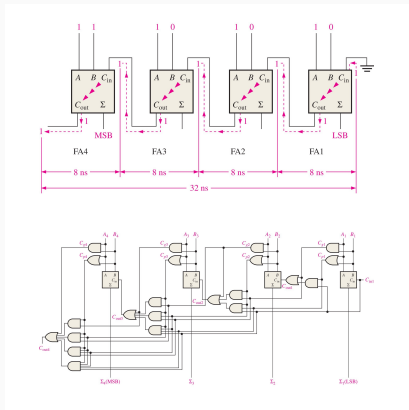

**Figure 9:** Propagation delays add serially in a full-adder with ripple carry topology.

# Half-Adders and Full-Adders, Ripple-Carry

 


**Figure 10:** Two 4-bit FA connected to form an 8-bit FA, accounting for carries.

# Comparators

---


# Comparators

 

**Figure 11:** The basic idea behind the comparator. (a) Review the truth table for the XNOR-gate, which is the conjugate of the XOR gate. (b) What is the function of the AND gate?




# Comparators

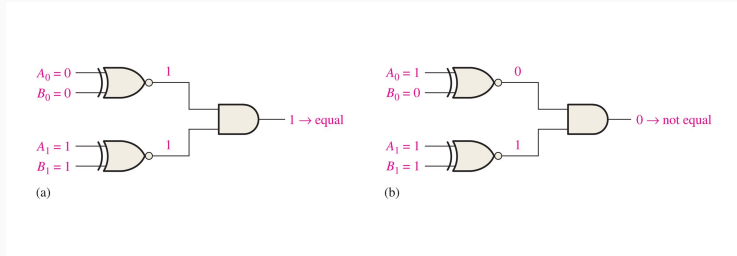


**Figure 12:** (a) Example of comparison of 2-bit binary numbers. (b) What is the truth table? (c) What is the logical representation of the function? (c) What is a logical representation for the inequality circuit?

# Comparators

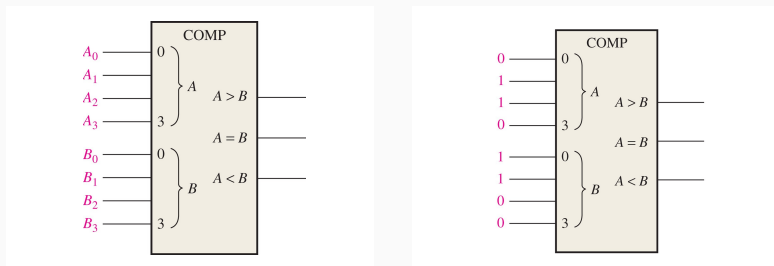

**Figure 13:** (Left) One *component* that is really 8 comparators linked to the same AND gate. (Right) What is the correct output? How to determine the inequality functions?

# Comparators

 


**Figure 14:** Try some simple cases: (a)  $A = 00$  and  $B = 01$ , (b)  $A = 10$  and  $B = 01$ .

# Decoders


---

# Decoders

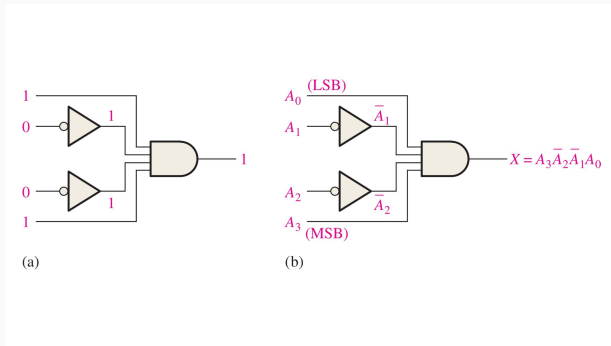

**Figure 15:** The binary decoder circuit for 9. This circuit is true if the binary number is 1001. (Pay attention to the order of MSB and LSB).

# Decoders

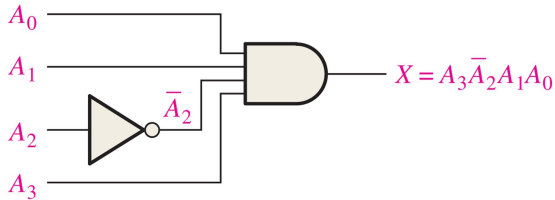

**Figure 16:** (a) Which binary number is being decoded here? (b) What would it take to decode all binary numbers of  $n$  bits?

**TABLE 6-4**

Decoding functions and truth table for a 4-line-to-16-line (1-of-16) decoder with active-LOW outputs.

Decimal Digit	Binary Inputs				Decoding Function	Outputs															
	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>		0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	0	0	$\overline{A_3}\overline{A_2}\overline{A_1}\overline{A_0}$	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1	0	0	0	1	$\overline{A_3}\overline{A_2}\overline{A_1}A_0$	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1
2	0	0	1	0	$\overline{A_3}\overline{A_2}A_1\overline{A_0}$	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1
3	0	0	1	1	$\overline{A_3}\overline{A_2}A_1A_0$	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1
4	0	1	0	0	$\overline{A_3}A_2\overline{A_1}\overline{A_0}$	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1
5	0	1	0	1	$\overline{A_3}A_2\overline{A_1}A_0$	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1
6	0	1	1	0	$\overline{A_3}A_2A_1\overline{A_0}$	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1
7	0	1	1	1	$\overline{A_3}A_2A_1A_0$	1	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1
8	1	0	0	0	$A_3\overline{A_2}\overline{A_1}\overline{A_0}$	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1
9	1	0	0	1	$A_3\overline{A_2}\overline{A_1}A_0$	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1
10	1	0	1	0	$A_3\overline{A_2}A_1\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1
11	1	0	1	1	$A_3\overline{A_2}A_1A_0$	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1
12	1	1	0	0	$A_3A_2\overline{A_1}\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1
13	1	1	0	1	$A_3A_2\overline{A_1}A_0$	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1
14	1	1	1	0	$A_3A_2A_1\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0
15	1	1	1	1	$A_3A_2A_1A_0$	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0


**Figure 17:** The decoding table for ACTIVE LOW 4-bit binary. Terms from linear algebra: this matrix has 0 trace, and is symmetric (we can exchange rows and columns).

# Encoders

---




# Encoders

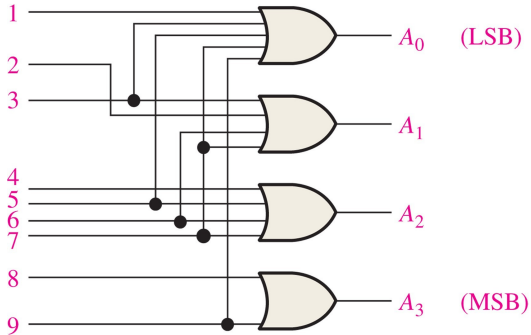

**Figure 18:** Recall the OR TT, and remember that this is a system in which there are forbidden or *don't care* states. Only one input line can be active at once.

# Encoders

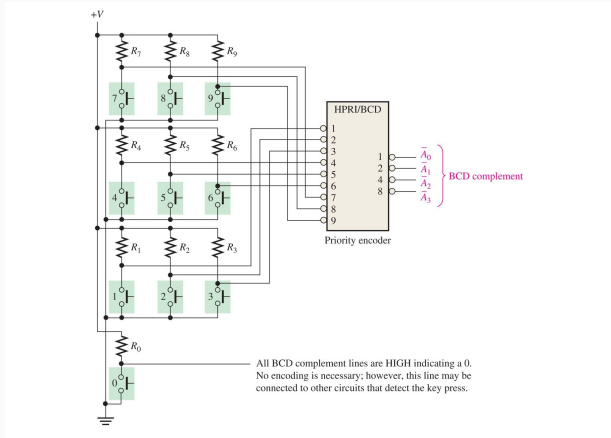


**Figure 19:** A keypad system. The binary encoder accepts only 9 digits because 0 is redundant. Note the use of *pull-up* resistors (recall LEDs operations).

# Multiplexers

---

# Multiplexers

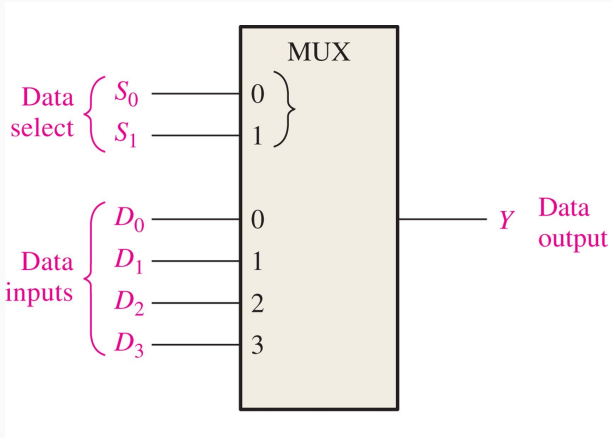

**Figure 20:** A general block diagram for a *multiplexer*. Parallel data input is successively rotated to the single output.


**TABLE 6–8**

Data selection for a 1-of-4-multiplexer.

Data-Select Inputs		Input Selected
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$


**Figure 21:** The desired TT for a 1-of-4 mux. The n-of-m jargon corresponds to inputs and outputs. We should also have *enable*, and one or more output lines.

# Multiplexers

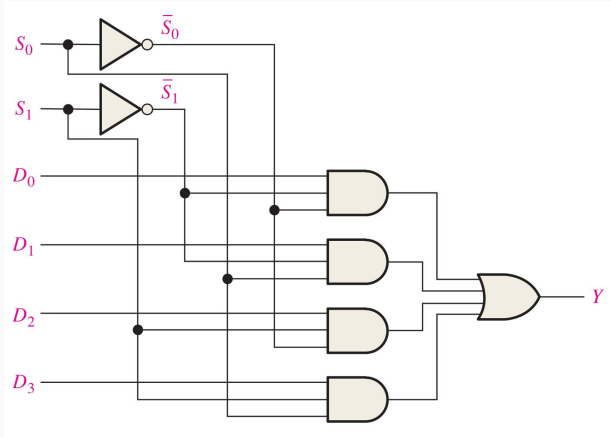


**Figure 22:** The AND-enable behavior is used in this 1-of-4 mux. Note the interconnections are the key to generating the right output logic.

# Multiplexers

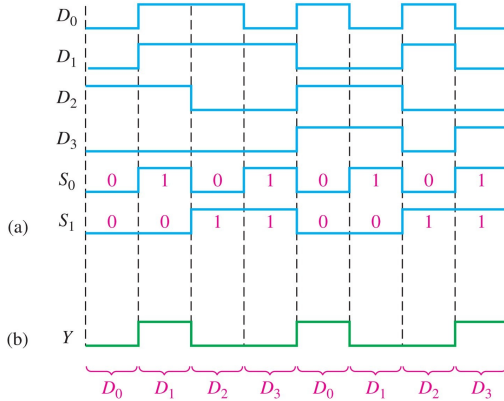

**Figure 23:** Exercise: verify the timing diagram output  $Y$  follows the 1-of-4 pattern. The data-select lines follow a 2-bit *counter* (coming soon).


# Multiplexers

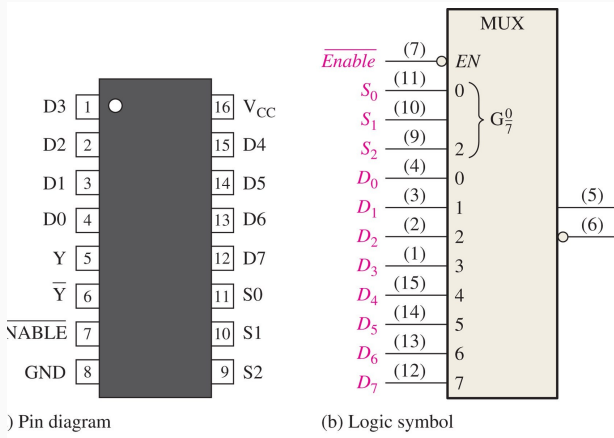

**Figure 24:** Active LOW enabled, 1-of-8 mux with complemented output.




# Multiplexers

 

**Figure 25:** Active LOW enabled, 1-of-8 mux with complemented output, connected to another one. The overall system acts as a 1-of-16 with 4 data select lines.


# Multiplexers

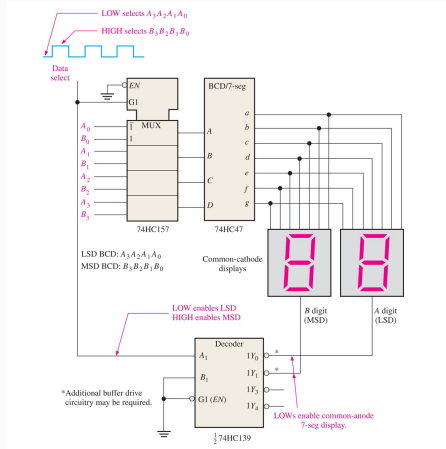

**Figure 26:** In this example, the mux is a *quad* 1-of-2, to help switch between binary numbers A and B. The BCD decoder converts the inputs, and the 2-to-4 decoder grounds either display.

# Multiplexers

6-9		
Inputs		Output
$A_1$	$A_0$	$Y$
0	0	0
0	1	1
1	0	0
1	1	1
0	0	0
0	1	1
1	0	1
1	1	0

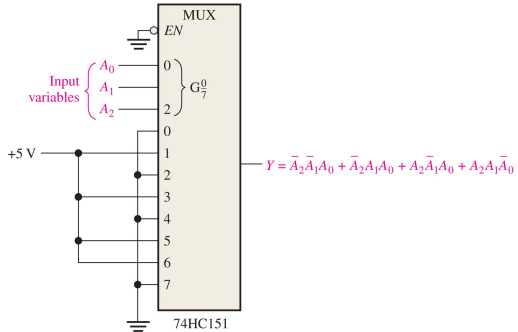


**Figure 27:** A mux can also be used to create any domain-N logic-function, provided we can connect HIGH and LOW to the desired input lines. Do you see the pattern?

# Demultiplexers


---

# Demultiplexers

 


**Figure 28:** The reverse operation to a multiplexer is a demultiplexer, or demux. Note the AND-enable is still there on the input line, but we need 4 ANDs: 1 for each possible input data line on the mux.

# Demultiplexers

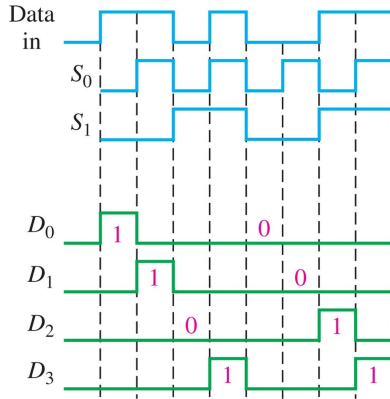

**Figure 29:** One data line in and four data lines out. *Note the cadence:* we cannot know what  $D_1$  is until we know what  $D_0$  is...

# Demultiplexers

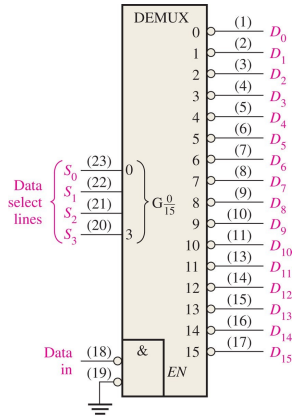

**Figure 30:** A decoder is very similar to a demux, but it has to have the data input lines at the bottom left.

## Conclusion

---



### Functions of Combinatorial Logic

**Reading:** 6-1 - 6-6 (Tuesday)

**Reading:** 6-7 - 6-11 (Thursday)

1. Half-Adders and Full-Adders
  - Example from study guide
  - Propagation delays
2. Comparators
  - The XNOR gate
  - Multi-bit comparators
  - Inequalities
3. Decoders/Encoders
  - Binary to decimal circuits
  - Decimal to binary circuits
4. Multiplexing and Demultiplexing