

# Tuesday Reading Assessment: Chapter 6

Prof. Jordan C. Hanson

March 31, 2020

## 1 Functions of Combinatorial Logic: Adders/Subtractors, Comparators, and Decoders/Encoders

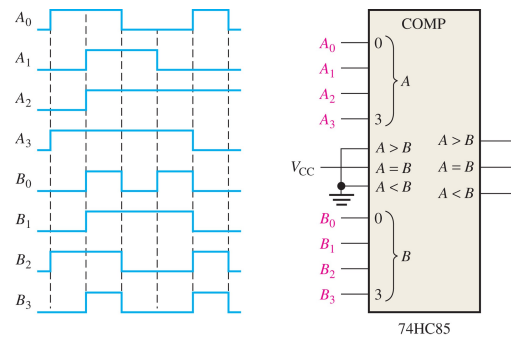


Figure 1: A logic circuit collecting two 4-bit binary numbers, with (effectively) one output.

- Given the input timing diagram in Fig. 1, what is the output waveform of the logic circuit?
- Figure 2 resembles a 4-bit FA (full adder). (a) The middle row of gates are XNOR gates. Show that  $B \text{ XNOR HIGH}$  equals  $B$ , and that  $B \text{ XNOR LOW}$  equals  $\text{NOT } B$ . (b) Taking  $A$  and  $B$  data from the first time bin in Fig. 1 (left), compute the  $\Sigma$  outputs if  $\overline{\text{Add/Subt}}$  is HIGH. (c) What would the outputs be if  $\overline{\text{Add/Subt}}$  is LOW?

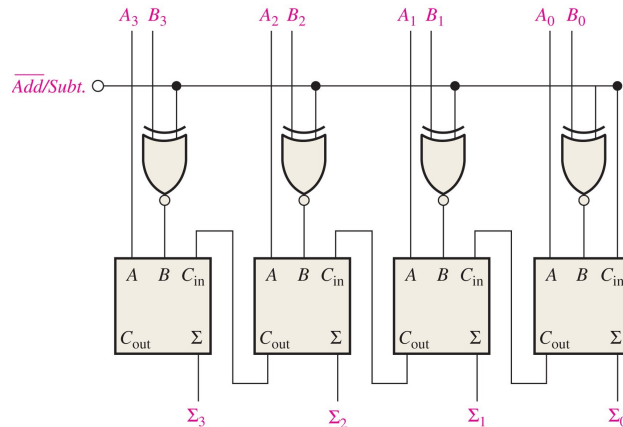


Figure 2: A 4-bit FA with an additional feature.