

COMPUTER LOGIC AND DIGITAL CIRCUIT DESIGN (PHYS306/COSC330): UNIT 1.1

Jordan Hanson

February 1, 2018

Whittier College Department of Physics and Astronomy

SUMMARY

Reading: Digital Fundamentals (DF) Ch. 1 (see Moodle)

1. Analog and Digital - RC filters and LC resonators
2. Introduction to digital concepts
3. Transistor radio...go!

Homework: exercises 1-20 Ch. 1 (DF)

Note: in each lecture I will have a *final battle* problem, which is meant to be harder. I will try to end the class on these types of problems, and if we do not solve it together, we can think about it for next time, or finish it on the homework.

Bonus Essay assignment: If you submit a 10-page paper on the history of computer science, including references from both online and library sources by the end of the semester, I will replace your lowest midterm score with the grade of the paper. Example topics:

- George Boole and the development of Boolean logic. What prompted this study?
- Bell Labs and the development of the transistor
- The first companies of silicon valley, the nobel prize, and the integrated circuit

Before beginning the essay, please make an appointment with me in office hours so that we may agree upon a topic.

ANALOG AND DIGITAL

The main topic of this course is *digital* electronics. What is the distinction between *digital* and *analog*? It is helpful to have a lesson in analog circuits, and then a lesson in digital circuits, for comparison.

One set of examples of analog circuits is RC/LC filters. We must apply *Ohm's Law* (Eq. 1) and *Kirchhoff's Rules* (Eqs. 2-3) to understand these circuits, so let's review those.

$$V = IR \quad (1)$$

$$\sum_{i, \text{node}}^N j_i = 0 \quad (2)$$

$$\sum_{i, \text{loop}}^N v_i = 0 \quad (3)$$

A node: a point in a circuit where conductors meet.

A loop: a path in a circuit that returns to the same node.

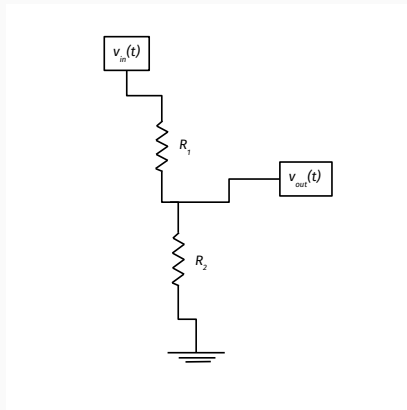


Figure 1: A two-resistor voltage divider.

- Using Ohm's Law, find expressions for $v_{\text{in}}(t)$ and $v_{\text{out}}(t)$ in terms of the resistances and the current.
- Take the ratio of the output voltage to the input voltage to find the **transfer function**, $H(t)$.
- Volunteer to board?

Answer:

$$H(t) = \frac{R_2}{R_1 + R_2} \quad (4)$$

In other words, the circuit does not change the time-domain properties of the signal, just the *amplitude*.

Can we replace a resistor with another component to *filter* signals based on time-domain properties?

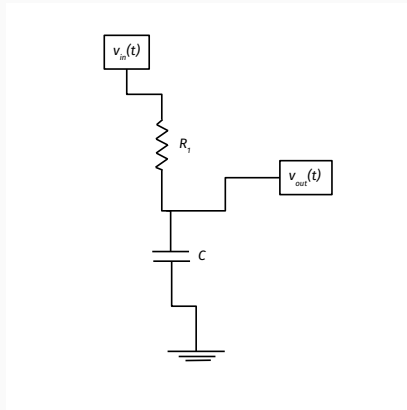


Figure 2: A single-pole low-pass RC filter. What is the resistance or impedance of a capacitor?

We need a math tool, the Fourier transform:

$$\mathcal{F}(f(t)) = \tilde{F}(\omega) = \int_{-\infty}^{\infty} f(t)e^{-j\omega t} dt \quad (5)$$

$$f(t) = g'(t) \quad (6)$$

$$\tilde{F}(\omega) = g(t)e^{-j\omega t} \Big|_{-\infty}^{\infty} + j\omega \int_{\infty}^{-\infty} g(t)e^{-j\omega t} dt \quad (7)$$

$$\mathcal{F}(g'(t)) = j\omega \mathcal{F}(g(t)) \quad (8)$$

After integrating by parts we find that the Fourier transform of a derivative of a function is the imaginary unit times the angular frequency times the Fourier transform of the function. **Note that throughout this course j is the imaginary unit. This is common in engineering texts.**

Impedance of a capacitor:

$$C = \frac{q}{V} \quad (9)$$

$$VC = q \quad (10)$$

$$C \frac{dV}{dt} = \frac{dq}{dt} = i(t) \quad (11)$$

$$\tilde{i}(\omega) = j\omega C \tilde{V}(\omega) \quad (12)$$

$$\frac{\tilde{V}(\omega)}{\tilde{i}(\omega)} = \frac{1}{j\omega C} \quad (13)$$

Using Ohm's Law, we identify the impedance as

$$\boxed{Z_C = \frac{1}{j\omega C}} \quad (14)$$

Repeat the earlier exercise, but with the new circuit:

- Using Ohm's Law, find expressions for $v_{\text{in}}(t)$ and $v_{\text{out}}(t)$ in terms of the impedances and the current.
- Take the ratio of the output voltage to the input voltage to find the **transfer function**, $H(t)$.
- Volunteer to board?

Answer:

$$M_{LP}(\omega) = \sqrt{\frac{\omega_0^2}{\omega^2 + \omega_0^2}} \quad (15)$$

$$\phi_{LP}(\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right) \quad (16)$$

The transfer function of this circuit depends on frequency in the following way:

1. $\omega \ll \omega_0$, $M_{LP} \approx 1$, $\phi_{LP} \approx 0$
2. $\omega \gg \omega_0$, $M_{LP} \approx 0$, $\phi_{LP} \approx -90^\circ$

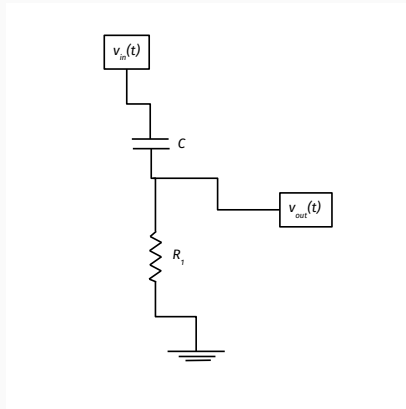


Figure 3: A single-pole high-pass RC filter. Can we repeat this process, only with the capacitor and resistor exchanged?

Answer:

$$M_{HP}(\omega) = \sqrt{\frac{\omega^2}{\omega^2 + \omega_0^2}} \quad (17)$$

$$\phi_{HP}(\omega) = \tan^{-1} \left(\frac{\omega_0}{\omega} \right) \quad (18)$$

The transfer function of this circuit depends on frequency in the following way:

1. $\omega \ll \omega_0$, $M_{HP} \approx 0$, $\phi_{HP} \approx 90^\circ$
2. $\omega \gg \omega_0$, $M_{HP} \approx 1$, $\phi_{HP} \approx 0$

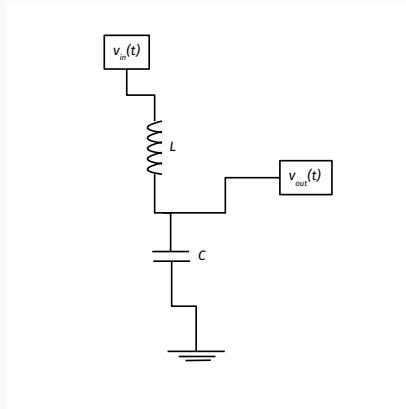


Figure 4: A simple LC-resonator (two-pole). What is the impedance of an inductor?

Impedance of an inductor:

$$L = \frac{d\phi}{di} \quad (19)$$

$$L = \frac{d\phi}{dt} \frac{dt}{di} = v/i'(t) \quad (20)$$

$$\tilde{v}(\omega) = j\omega L \tilde{i}(\omega) \quad (21)$$

So we can read off the impedance of the inductor:

$$\boxed{Z_L = j\omega L} \quad (22)$$

Following the same model, but with new impedances, we find Eq. 17 below by defining a *resonance frequency* $\omega_R^{-2} = LC$.

$$M_{LC}(\omega) = \frac{\omega_R^2}{\omega_R^2 - \omega^2} = \frac{\omega_R^2}{(\omega_R - \omega)(\omega_R + \omega)} \quad (23)$$

Analog circuits

- Continuous functions of voltage and current representing continuous data
- Application of complex analysis

-
- Cannot be stored, copied or transmitted quickly and efficiently
 - Requires knowledge of every frequency (bandwidth issues)
 - Cannot be transmitted easily (noise issues)

Digital circuits

- Discrete functions of voltage and current representing coded data
- Application of Boolean logic

-
- Must sample enough information to reproduce analog signals

Music is an obvious example: storing music on a vinyl record creates a groove in the material of the record that follows the pressure wave pattern of the sound. At no point are any frequencies lost, unless the record is scratched. When music is stored digitally, the sample rate affects quality, but with a large sample rate, the music is indistinguishable from the record player. Plus, the music can be perfectly copied or transmitted.

INTRODUCTION TO DIGITAL CONCEPTS

Recall from the low and high pass filter examples:

1. $\omega \ll \omega_0, M_{\text{HP}} \approx 0, \phi_{\text{HP}} \approx 90^\circ$
 2. $\omega \gg \omega_0, M_{\text{HP}} \approx 1, \phi_{\text{HP}} \approx 0$
-

1. $\omega \ll \omega_0, M_{\text{LP}} \approx 1, \phi_{\text{LP}} \approx 0$
2. $\omega \gg \omega_0, M_{\text{LP}} \approx 0, \phi_{\text{LP}} \approx -90^\circ$

What if instead of a frequency-based filter, we had an amplitude-based filter? (Also known as transistors...stay tuned).

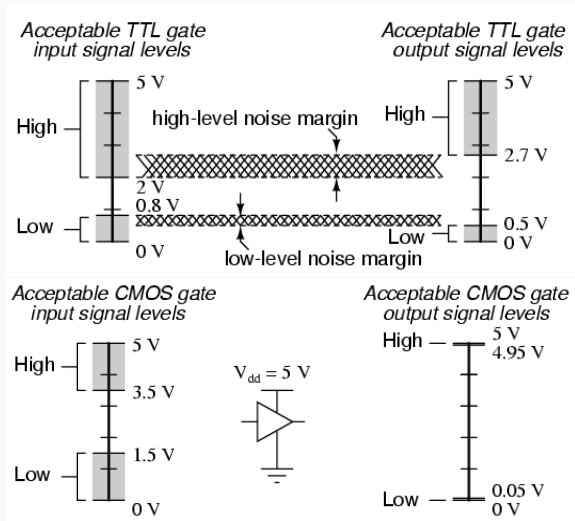


Figure 5: TTL and CMOS logic levels in integrated circuits today.

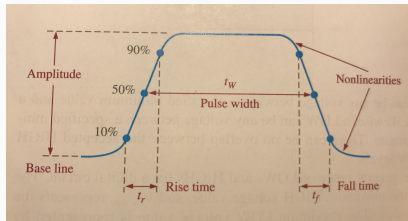


Figure 6: Properties of the logic pulse: rise and fall times, amplitude and non-linearities.

From where do the non-linearities arise? Turns out the Fourier transform of a square wave $s(t)$ with period T is a “sync” function ($2\pi\nu = \omega$):

$$\mathcal{F}(s(t)) = \tilde{S}(\nu) = \frac{\sin(\pi\nu T)}{\pi\nu} \quad (24)$$

From where do the non-linearities arise? Turns out the Fourier transform of a square wave $s(t)$ with period T is a “sync” function ($2\pi\nu = \omega$):

$$\mathcal{F}(s(t)) = \tilde{S}(\nu) = \frac{\sin(\pi\nu T)}{\pi\nu} \quad (25)$$

The **convolution theorem** states that if a signal is being filtered, the transfer function of that filter is being multiplied with the Fourier transform of the signal in the Fourier domain. Let's *low-pass filter* the sync function:

$$\tilde{S}(\nu)H_{\text{LP}}(\omega) = \frac{\sin(\pi\nu T)}{\pi\nu} \sqrt{\frac{\omega_0^2}{\omega^2 + \omega_0^2}} \quad (26)$$

$$\tilde{S}(\nu)H_{\text{LP}}(\omega) = \frac{\sin(\pi\nu T)}{\pi\nu(1 + (2\pi\nu\tau)^2)^{1/2}}, \tau = \omega_0^{-1} \quad (27)$$

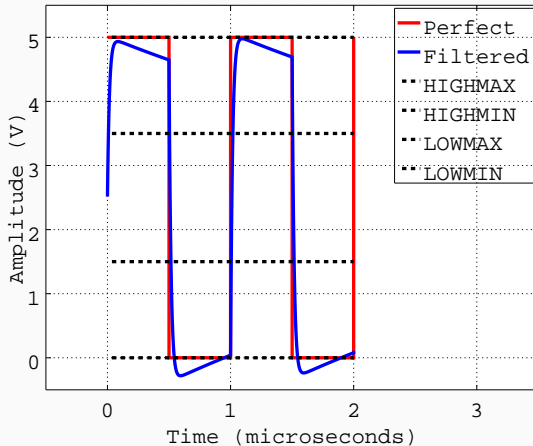


Figure 7: CMOS logic pulse filtered to remove frequencies above 0.01 MHz and below 2 MHz for a 1 MHz clock frequency.

Fourier transform:

$$\mathcal{F}(f(t)) = \int_{-\infty}^{\infty} f(t) \exp(-2\pi j\nu t) dt \quad (28)$$

In-class exercises. Evaluate the Fourier transform of each of the following functions/distributions:

1. $f(t) = \delta(t - t_0)$
2. $f(t) = \exp(-at)$, for $t \geq 0$, 0 for $t < 0$

Now compute the modulus-squared for each result: $z^*z = |z|^2$.
What is the frequency-dependence of each?

Pulse-waveform vocabulary:

1. **Period** - Time required for a repeating signal to return to original state.
2. **Frequency** - Inverse of the period.
3. **Pulse width** - Width of time between identical signal values
4. **Rise time** - Time required for the signal to rise from 10% to 90% of the amplitude
5. **Fall time** - Similar to fall time but for amplitude decrease
6. **Duty cycle** - Pulse width divided by period

Major feature of digital circuit components: *any* voltage between HIGHMAX and HIGHMIN is HIGH, and *any* voltage between LOWMAX and LOWMIN is LOW. Issues of bandwidth and filtering are nullified because the circuit will perform the correct action *regardless of these effects*.

HIGH	1
LOW	0

Table 1: Digital circuits strategically neglect the analog nature of the voltage inputs.

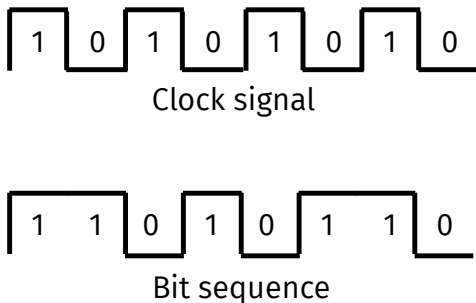


Figure 8: The clock simply switches between HIGH and LOW periodically. Normal data sequences are strings of *bits*. In this case, we have 11010110.

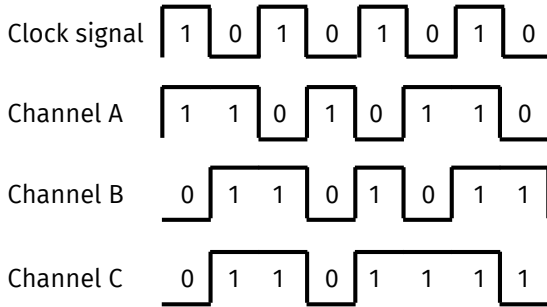


Figure 9: A timing diagram. A display of the synchronized bit sequences of multiple data channels.

Logic operations:
NOT, AND, OR

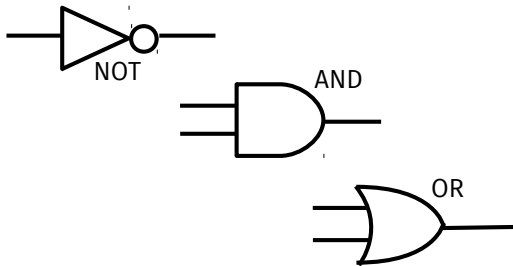


Figure 10: Bit sequences can be inputs to **logic operations**, performed by *gates* (more later).

Input	Output
1	0
0	1

Table 2: NOT truth table.

Input1	Input2	Output
1	1	1
1	0	1
0	1	1
0	0	0

Table 4: OR truth table.

Input1	Input2	Output
1	1	1
1	0	0
0	1	0
0	0	0

Table 3: AND truth table.

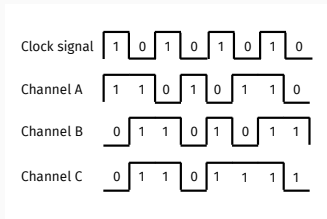


Figure 11: Bit sequences → logic operations → new bit sequences.

Write down the following bit sequences:

1. NOT A
2. A OR Clock
3. A AND B
4. A AND (B OR C)

Volunteers to board?

1. NOT A
2. A OR Clock
3. A AND B
4. A AND (B OR C)

How would you express the final exercise in terms of gates representing logic operations and bit sequences as inputs?

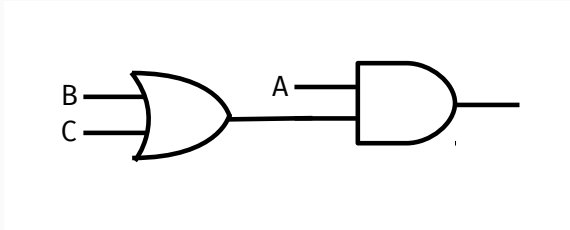


Figure 12: Solution: do the grouping symbol first, as in order of operations.

Compose a circuit of gates that produces the following bit sequences:

1. $(\text{NOT } (A \text{ AND } B)) \text{ OR } C$
2. $\text{NOT } A \text{ AND } B$
3. $A \text{ AND } B \text{ AND } C \text{ AND } D$
4. $(A \text{ OR } B) \text{ AND } (A \text{ OR } B)$

A few more logic operators:

1. **Comparator**
2. Adder
3. Encoder
4. Decoder
5. Shift register
6. Flip-flop
7. Multiplexer
8. Demultiplexer
9. Counter

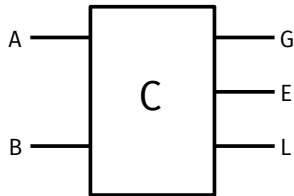


Figure 13: A comparator compares bit sequences A and B, and raises G to HIGH if A represents a number greater than B, E if they are equal, and L if A is less than B.

A few more logic operators:

1. Comparator
2. **Adder**
3. Encoder
4. Decoder
5. Shift register
6. Flip-flop
7. Multiplexer
8. Demultiplexer
9. Counter

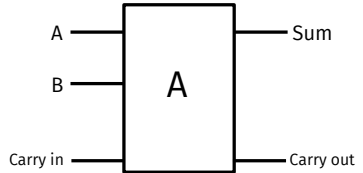


Figure 14: An adder adds two binary numbers (bit sequences A and B here) in the same way we add numbers on paper. We carry powers of 10 (2) on paper (in binary).

Group board exercise: Compose a circuit that records adds two inputs, compares the result to a third input, and has an output of HIGH if the sum of the first two inputs is greater than the third input. *Use more than one adder, but assume that the numbers are small enough to not need the last C_{out} .*

But wait, how can the adder physically know how to add if it receives the digits one by one? Don't all these elements operate on clock cycles?

Good question. We need the concept of *serial data* versus *parallel data*.

- **Serial data:** one connection, many clock cycles per bit sequence.
- **Parallel data:** many connections, one clock cycle per bit sequence.

A few more logic operators:

1. Comparator
2. Adder
3. **Encoder**
4. Decoder
5. Shift register
6. Flip-flop
7. Multiplexer
8. Demultiplexer
9. Counter

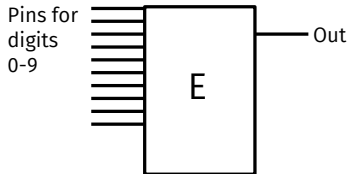


Figure 15: The encoder has preset pins corresponding to (for example) digits 0-9, and the output bit sequence is a binary representation of the input that is raised HIGH.

Group board exercise - final battle: Compose a circuit that takes as inputs two numbers 0-9, and adds them. The output of the circuit is HIGH if and only if the result is between 8 and 12, inclusive.

LAB TOUR, AND INTRODUCTION TO LAB PROJECT 1

LAB TOUR, AND INTRODUCTION TO LAB PROJECT 1

Our first project is an AM transistor radio (pictured at right).

Goals:

- Share the experience of diving into an electronics project blind
- Understand why transistors revolutionized this device
- Learn how a transistor works
- Learn how to use test equipment like DVMs
- Learn how to solder



Figure 16: The TecSun 2P3 transistor radio.

CONCLUSION

Reading: Digital Fundamentals (DF) Ch. 1 (see Moodle)

1. Analog and Digital - RC filters and LC resonators
2. Introduction to digital concepts
3. Transistor radio...go!

Homework: exercises 1-20 Ch. 1 (DF)

Note: in each lecture I will have a *final battle* problem, which is meant to be harder. I will try to end the class on these types of problems, and if we do not solve it together, we can think about it for next time, or finish it on the homework.