
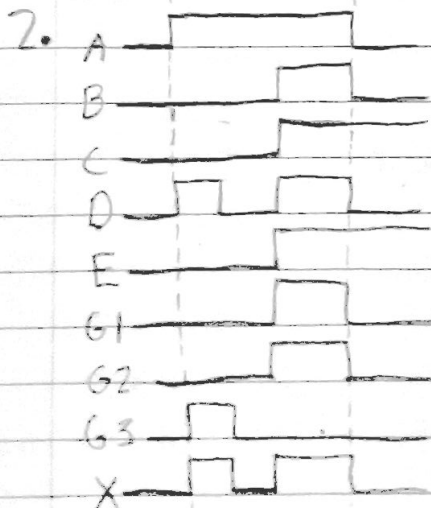


Midterm 2

Ch 5

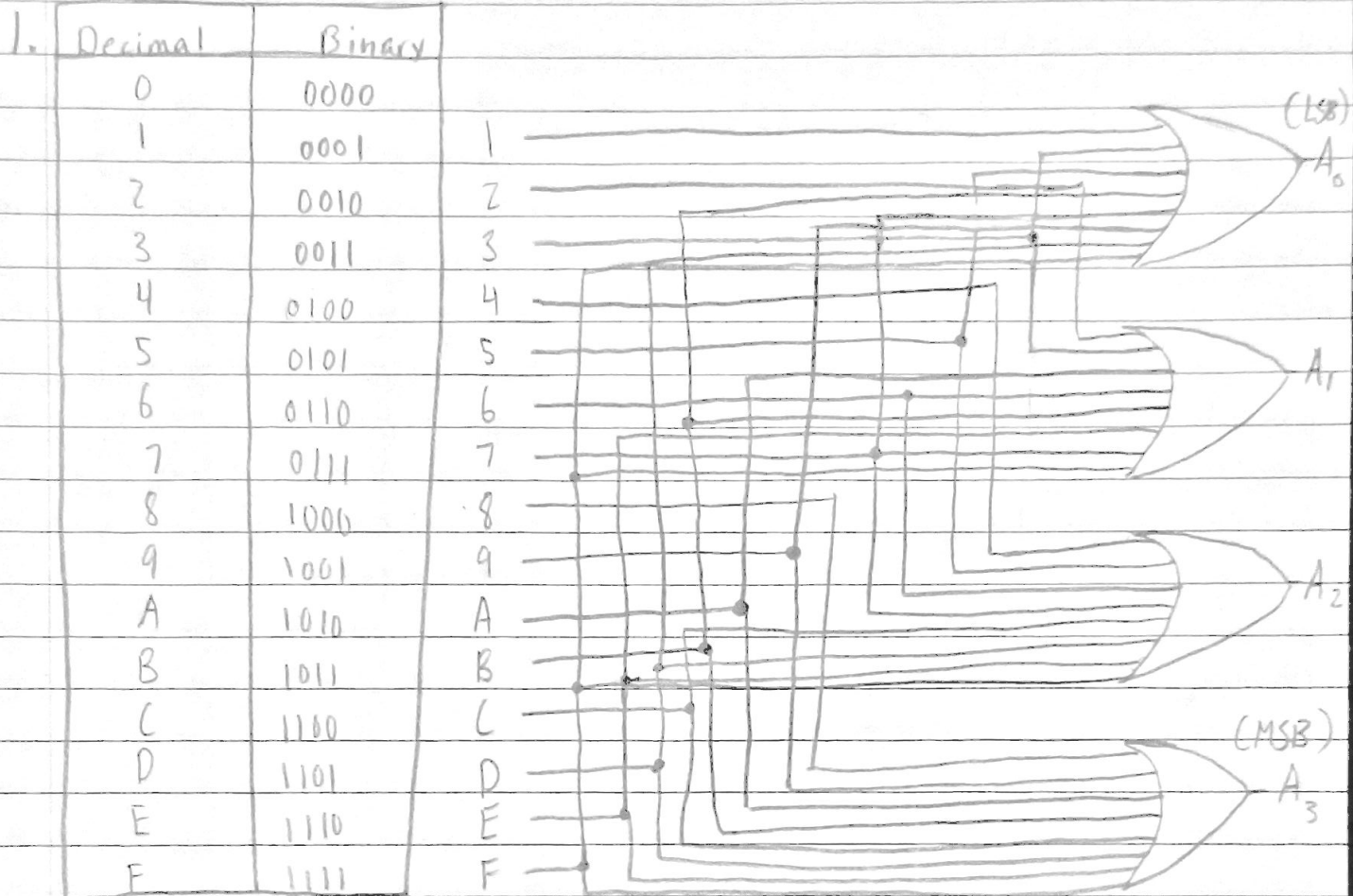

Either G1 or G2 is faulty, only providing a constant LOW. This would explain why the X output in the figure remains low even though G1 and G2 are supposed to be HIGH. (output open)