

# Computer Logic and Digital Circuit Design (PHYS306/COSC330): Week 1

---

Jordan Hanson

August 24, 2021

Whittier College Department of Physics and Astronomy

## Summary

---


1. Logic functions
  - Basic gate ideas
  - Combinatorial logic functions
  - Serial and parallel
2. Programmable logic (PL) vs. fixed integrated circuits (ICs)
3. Test instruments
  - Oscilloscope
  - Signal generator
  - Digital voltmeter and DC power supply

# Analog Circuits

---

# Analog Circuits


First of all, what is an *analog* circuit?

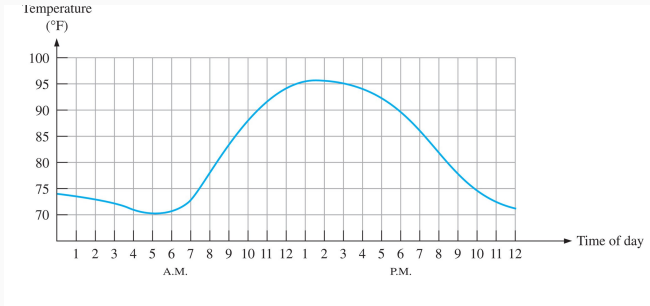

**Figure 1:** An example of an analog signal from a temperature sensor, converted from voltage.

# Analog Circuits

First of all, what is an *analog* circuit?

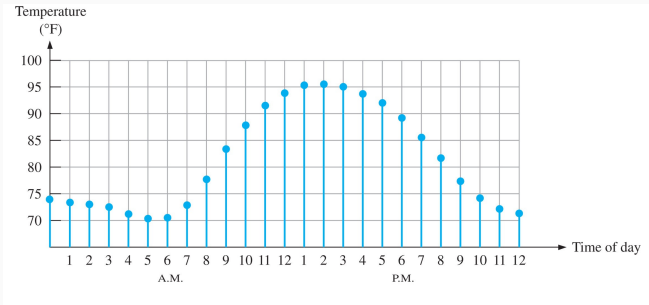


**Figure 2:** An example of that same signal, digitized and sampled.

Digital data forms the basis of computation:

- Noise issues, lossless transmission
- Constructed from *digits* ... 1 and 0

# Analog Circuits

First of all, what is an *analog* circuit?

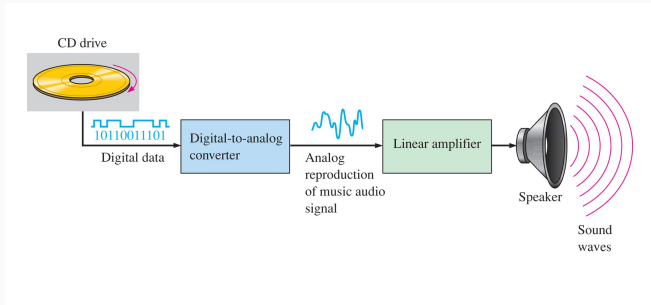

**Figure 3:** An example of a digital signal converted from binary to analog voltage signal.

# Analog Circuits

One set of examples of analog circuits is RC/LC filters. We must apply *Ohm's Law* (Eq. 1) and *Kirchhoff's Rules* (Eqs. 2-3) to understand these circuits, so let's review those.

$$V = IR \quad (1)$$


$$\sum_{i, \text{node}}^N j_i = 0 \quad (2)$$

$$\sum_{i, \text{loop}}^N v_i = 0 \quad (3)$$

**A node:** a point in a circuit where conductors meet.

**A loop:** a path in a circuit that returns to the same node.



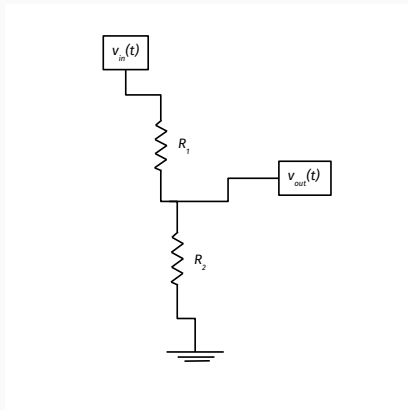

**Figure 4:** A two-resistor voltage divider.

- Using Ohm's Law, find expressions for  $v_{\text{in}}(t)$  and  $v_{\text{out}}(t)$  in terms of the resistances and the current.
- Take the ratio of the output voltage to the input voltage to find the **transfer function**,  $H(t)$ .

Answer:

$$H(t) = \frac{R_2}{R_1 + R_2} \quad (4)$$

Only the amplitude is affected:

- Original signal:  $s_{in}(t) = A \cos(2\pi ft + \phi)$
- New signal:  $s_{out}(t) = A \left( \frac{R_1}{R_1 + R_2} \right) \cos(2\pi ft + \phi)$

Other actions we can do in the time-domain:


- *Delay*: shift the signal in time
- *Filter*: change which frequencies are most powerful
- *Integral/derivative*: circuit output is proportional to the integral or derivative of input

# Logic Functions

---

# Logic Functions

How do we build up digital data from analog signals?

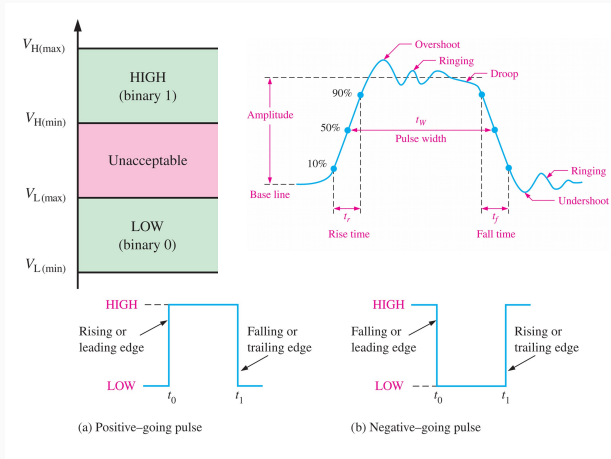


**Figure 5:** Logical "1" and "0."

Terminology for digital signals:


1. **Frequency**,  $f$  and **period**,  $T$ : Signals per second, time between signals ( $f = 1/T$ ).
2. **Pulse width**,  $t_W$ : time duration a pulse is HIGH.
3. **Duty cycle**:  $t_W/T \times 100\%$

# Logic Functions

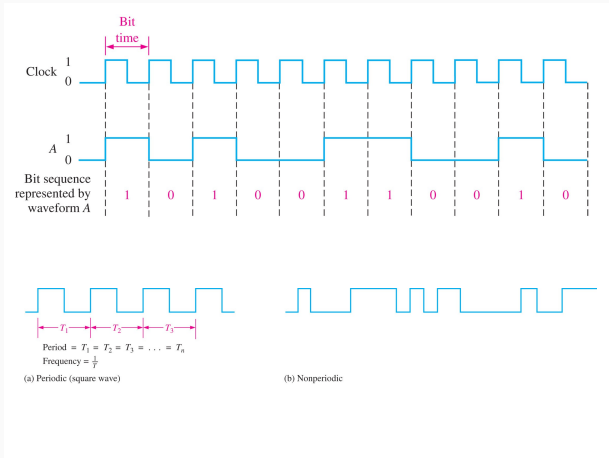

**Figure 6:** A clock signal is an example of a digital bitstream: alternating 1 and 0. It has a period and a frequency. Data can be *periodic* or *non-periodic*. (Professor: do some examples here).

# Logic Functions

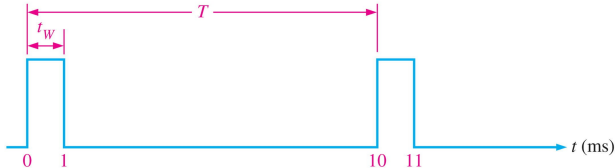


**Figure 7:** A periodic pulse demonstrating the concept of duty cycle.  
(Professor: do an example here and vary duty cycle).

**What is the duty cycle in Fig. 7? What is the frequency?**



# Logic Functions


Logic function: mapping digital inputs to outputs. A *timing diagram* displays three digital inputs.

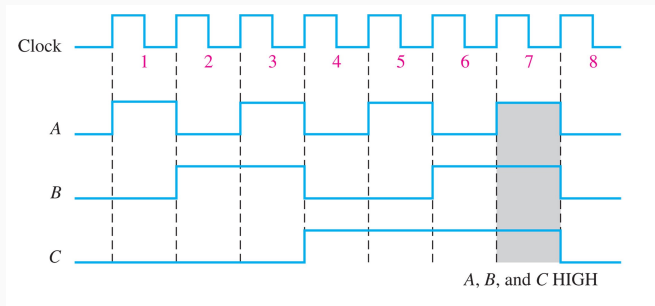

**Figure 8:** A logic function can be displayed as a timing diagram. Add a fourth input, labeled OUT. Suppose OUT is only high when A, B, and C are all high. Draw OUT versus time.

# Logic Functions


Logic gates: fundamental blocks of logic functions.

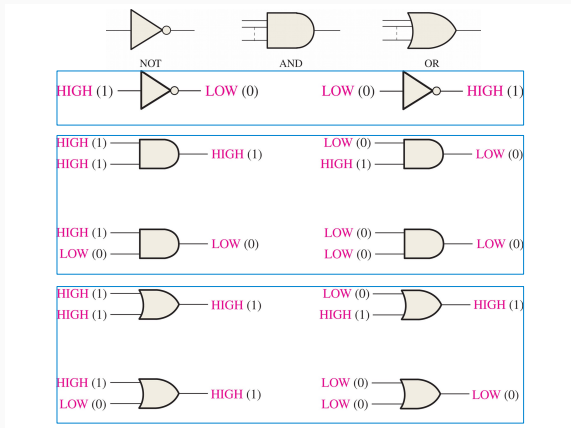

**Figure 9:** NOT, AND, and OR. These gates are built from transistors, and have *truth tables*.

# Logic Functions


Logic gates: combinatoric functions are built from gates.

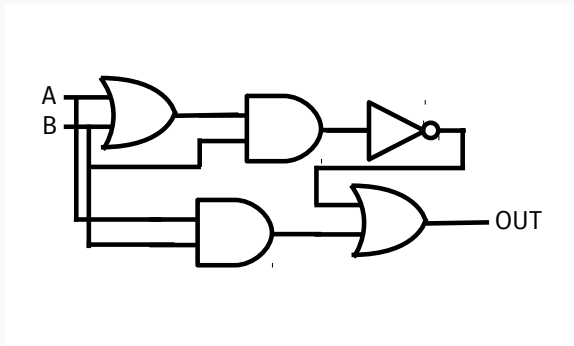

**Figure 10:** NOT, AND, and OR gates build up other functions. What function is being described here? What three states (values for A and B) would make OUT go high?

# Logic Functions


Logic gates: combinatoric functions are built from gates.

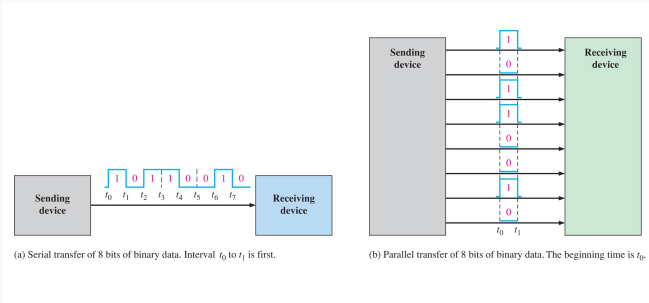


**Figure 11:** Combinatoric functions can exchange data in serial and parallel form.

## PL versus IC


---

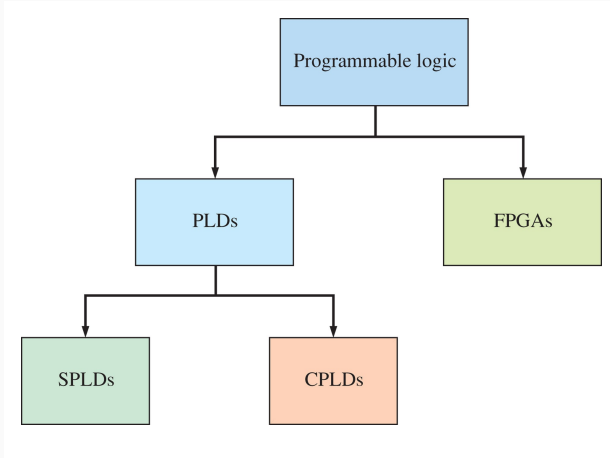

**Figure 12:** Programmable logic falls into several categories. (a) Programmable logic devices (PLDs), simple and complex. (b) Field Programmable Gate Arrays (FPGAs).

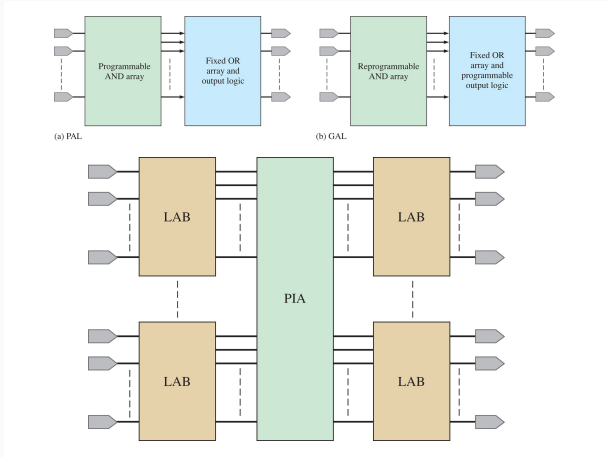


**Figure 13:** Programmable logic devices (PLDs), simple and complex. Combinatoric logic functions can be built using these systems.

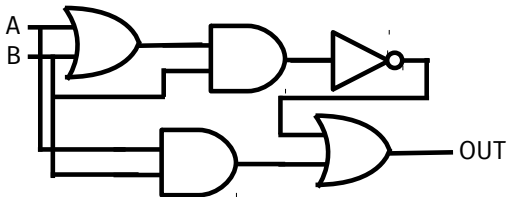


**Figure 14:** This function reduces to  $\bar{B} + AB$ .

SPLD could be used to temporarily create this function.



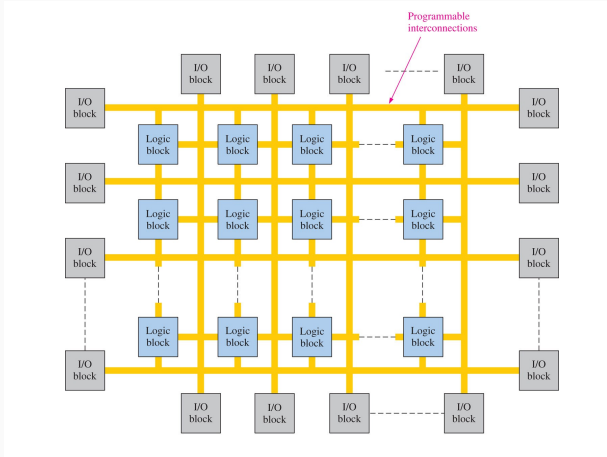

**Figure 15:** Field Programmable Gate Arrays (FPGAs) can be used to design vast, complex systems of logic functions.

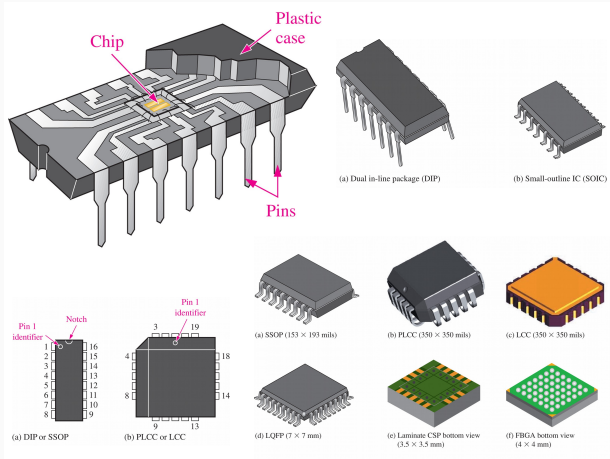


**Figure 16:** Various types of integrated circuits (ICs), that represent fixed combinatoric functions. They come in through-hole and surface mount varieties.

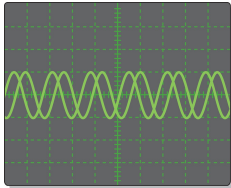
# Test Instruments

---

# Test Instruments




(a) Untriggered waveform display

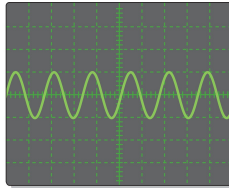

(b) Triggered waveform display


**Figure 17:** The oscilloscope plots digital and analog signals versus time. The scope needs to *trigger*.

# Test Instruments

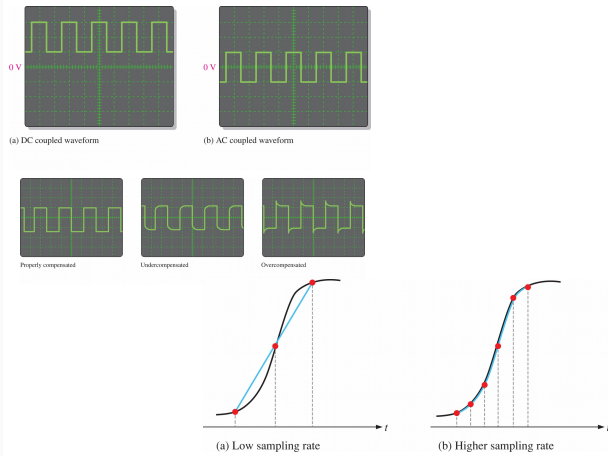

**Figure 18:** The scope needs to *sample* at a high enough sampling rate to compensate for frequency of data. There's also the issue of AC versus DC coupling. (Professor: do some examples here).

# Test Instruments

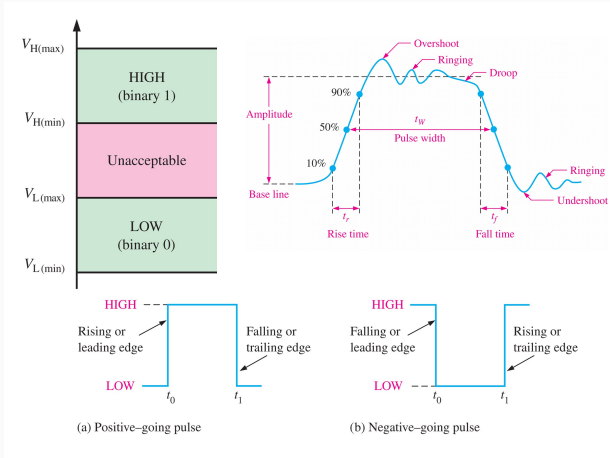

**Figure 19:** With this issue, we begin our laboratory activity.

## Conclusion

---

1. Logic functions
  - Basic gate ideas
  - Combinatorial logic functions
  - Serial and parallel
2. Programmable logic (PL) vs. fixed integrated circuits (ICs)
3. Test instruments
  - Oscilloscope
  - Signal generator
  - Digital voltmeter and DC power supply