

Tuesday Reading Assessment: Chapter 4

Prof. Jordan C. Hanson

March 5, 2020

1 Logic Circuits and Boolean Algebra

- (a) Write the boolean expression for the circuit in Fig. 1. (b) Convert the expression to S-SOP form, using $X + \bar{X} = 1$. What is the domain number?

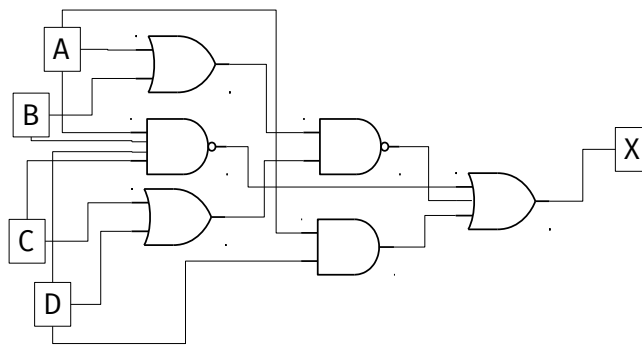


Figure 1: What is the logical expression for the output?

- Determine the truth table (TT) for the circuit in Fig. 1.