

due Friday, Sept. 24

use wavedrom.com

Roger Chen



9/17/2021

PHYS 306

Homework 3



Section 3-2 #8

8) Draw the net output waveform of this system (Figure 3-81).

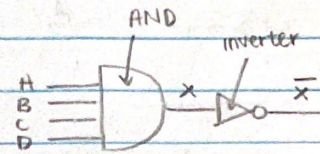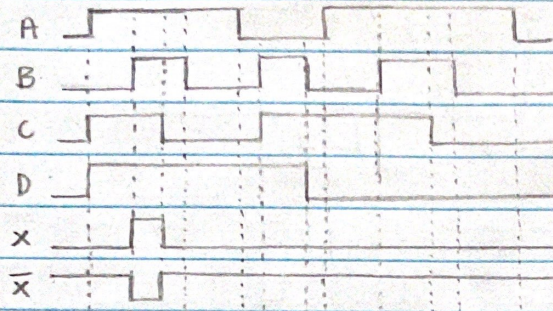



Section 3-3 #14

14) Draw the net output waveform (Figure 3-82)

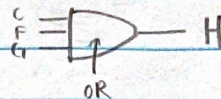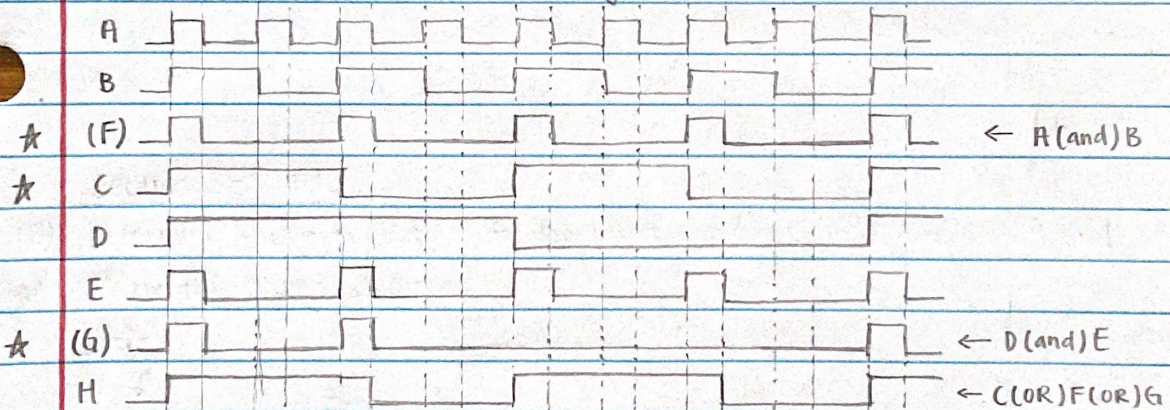

Section 3-4 # 18

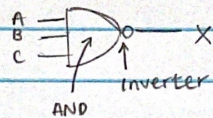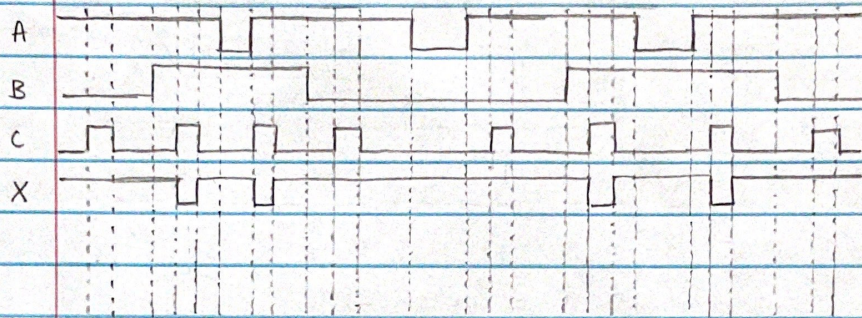- 18) Determine the gate output for the input waveforms in Figure 3-84 and draw the timing diagram



I have no idea how to use wavedrom so I gave up. Sorry :-