

Midterm 2 for COSC330/PHYS306 - Fall 2021

Dr. Jordan Hanson - Whittier College Dept. of Physics and Astronomy

November 21, 2021

1 Chapter 6 - Functions of Combinational Logic

1. Consider Fig. 1, in which a 4-bit adder is depicted. Assuming a uniform worst-case delay of 8 ns from carry-in to carry-out for each stage, the total delay is 32 ns. (a) At what maximum frequency can this circuit perform additions, if the delay must be less than a clock period? (b) What would the result in (a) be if the adder was extended to 8 bits? (c) Create a timing diagram showing the addition of the numbers in Fig. 1. **Bonus:** include the timing delays, and indicate the clock period.

a) $f_{\max} = \frac{1}{32 \text{ ns}}$
 $= 31.25 \text{ MHz}$

v) $f_{\max} = \frac{1}{64 \text{ ns}}$
 $= 15.625 \text{ MHz}$


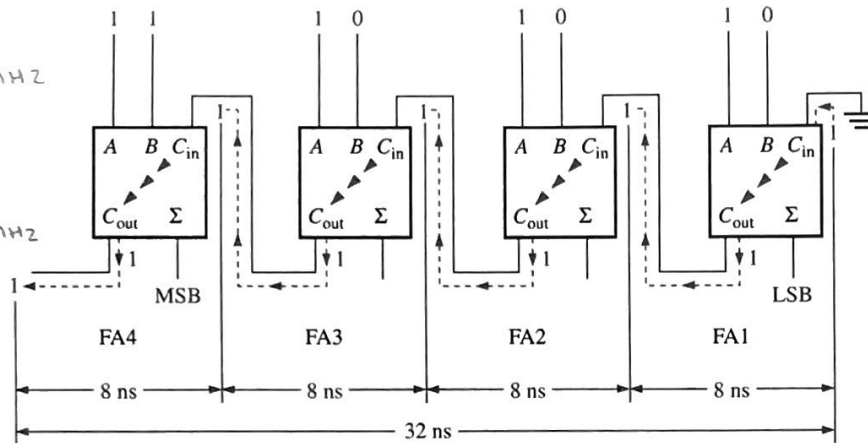
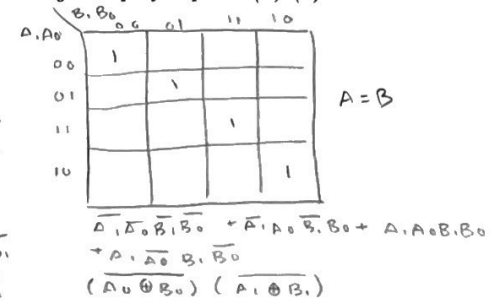


Figure 1: A schematic of a 4-bit adder with delays marked in nanoseconds.

2. Using AND, OR, XNOR, and inverter gates, (a) create a 2-bit comparator that yields True if $A > B$, (b) True if $A = B$, and (c) True if $A < B$. For each circuit, assume both A and B are 2-bit binary positive numbers. (d) Wrap this all into one circuit with three outputs and 4 inputs. *Hint: use Karnaugh maps for parts (a)-(c) to simplify the gates.*

a-c)


A_1	A_0	B_1	B_0	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	1	0	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	0	1
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	0
1	1	1	1	0	1	0

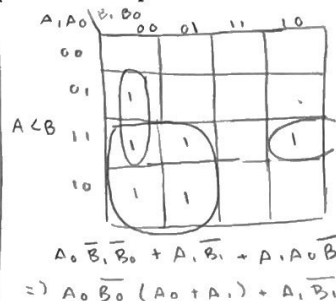



Truth table for $A < B$:

$A_1 A_0$	$B_1 B_0$	$A < B$
00	00	0
00	01	1
00	11	1
00	10	1
01	00	0
01	01	0
01	11	1
01	10	1
11	00	0
11	01	0
11	11	0
11	10	0
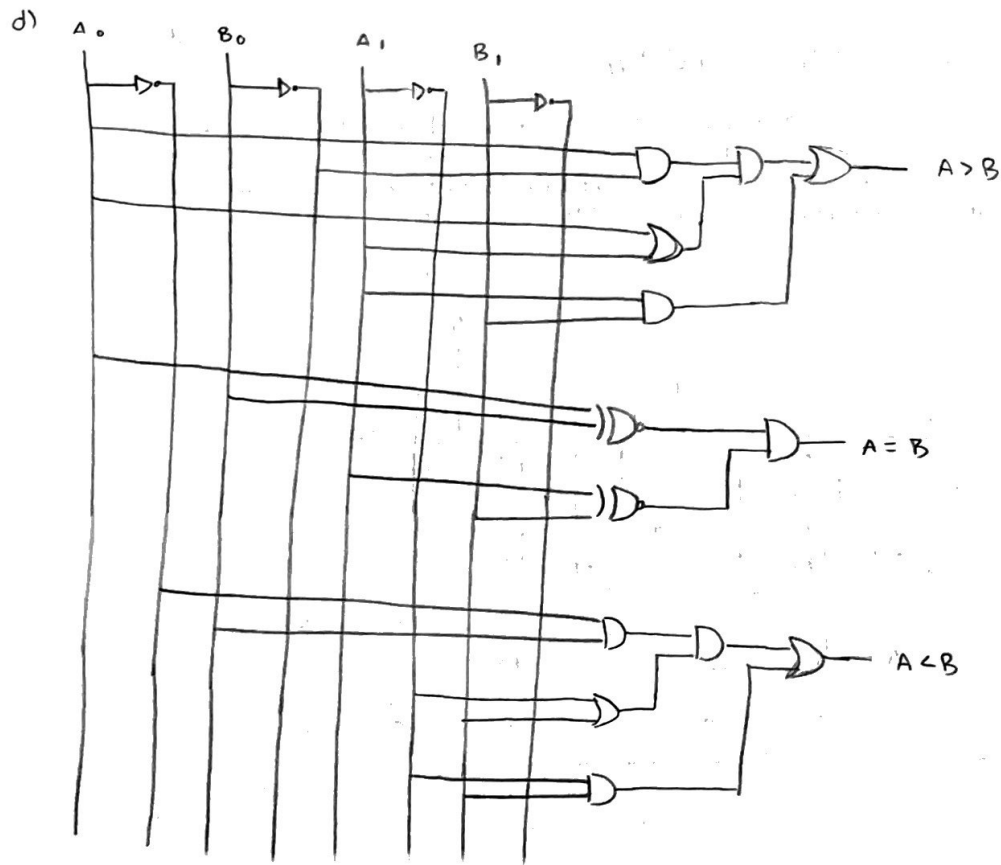
$$\begin{aligned} & \overline{A_1} \overline{A_0} B_0 + \overline{A_1} B_1 + \overline{A_0} B_1 B_0 \\ &= \overline{A_1} B_0 (\overline{A_0} + B_1) + \overline{A_0} B_1 \end{aligned}$$



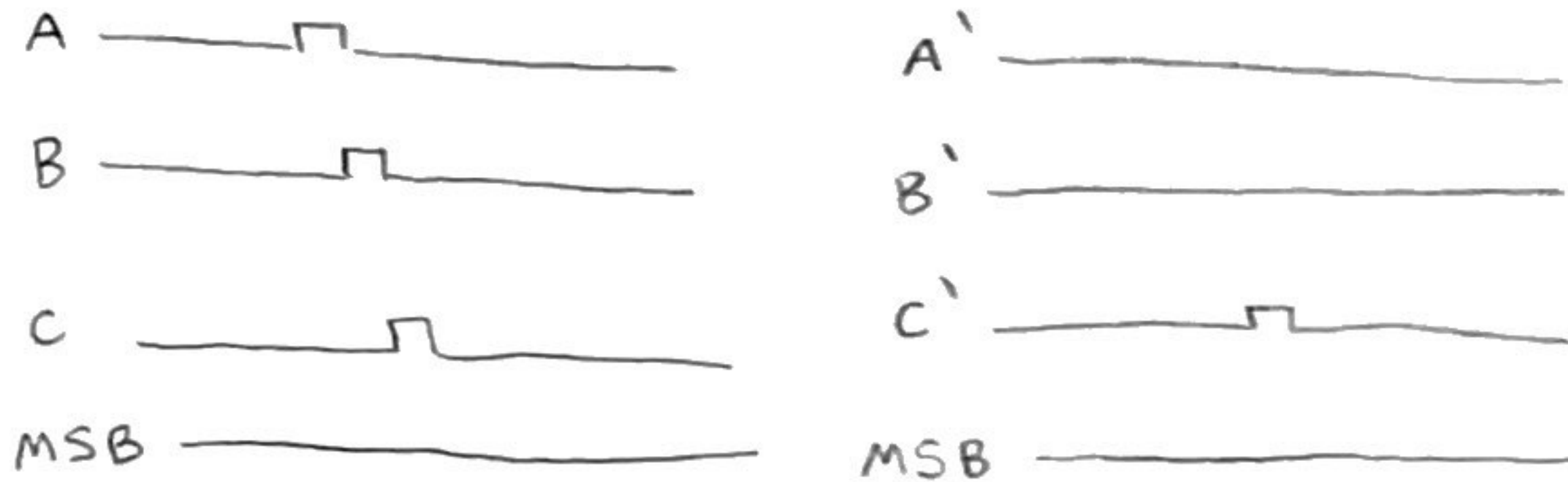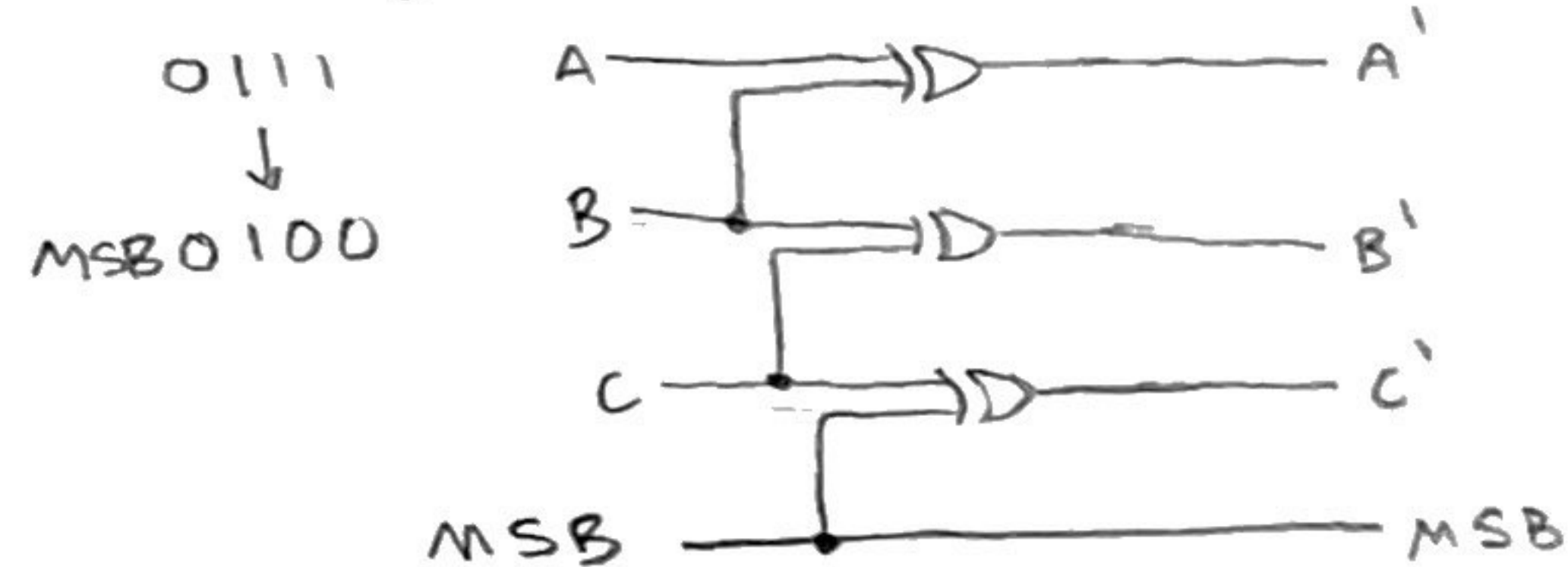3. Generate the logic gates that convert 4-bit gray code to 4-bit binary code, and show that it works with a timing diagram.



4. Consider Fig. 2, in which a decimal to binary conversion circuit is shown. (a) Add logic to the circuit such that it becomes a hexadecimal to binary converter. (b) Draw a logic symbol for this circuit with the correct number of inputs and outputs. (c) Connect two hex-to-bin converters to a symbolic 2-to-1 multiplexer with the correct number of data select line(s) to form a system that can send two-digit hex numbers over one output line.

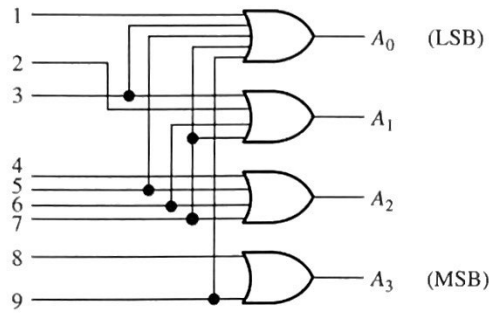


Figure 2: A decimal to binary encoder circuit.

2 Chapter 7 - Latches, Flip-flops, and Timers

1. Consider Fig. 3, in which a divide-by-four frequency divider is depicted with D flip-flops and a CLK signal. (a) Elaborate on this circuit to create a circuit that can divide the clock frequency by 2, 4, or 8. Show the flip-flops explicitly. (b) Develop a symbol for the 2-4-8-16 divider, with CLK signal input and four outputs (one each for $f/2$, $f/4$, $f/8$, and $f/8$, where f is the clock frequency). (c) Connect the symbol for the new part to a symbolic 4-to-1 multiplexer with the appropriate number of data select lines to form a clock division system. (d) Show with a timing diagram the output if the user changes the data select lines at least once. For parts (b)-(d), it is only necessary to show symbols rather than individual flip-flops.

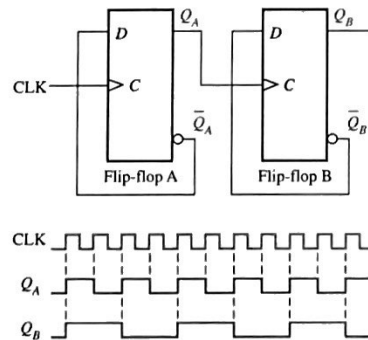


Figure 3: Two D flip-flops forming a frequency divider.

3 Chapters 8 and 9 - Shift Registers and Counters

1. Consider the timing diagram in Fig. 4. Using any combination of *shift registers* and supporting gates, create a circuit with 8-outputs that produces this timing diagram.


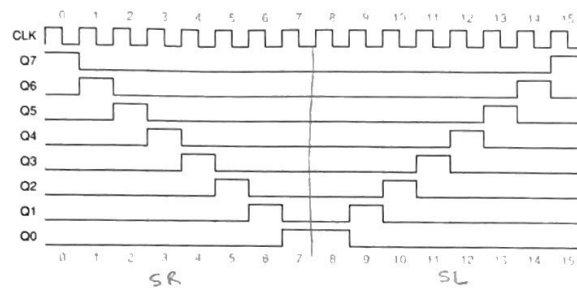


Figure 4: A waveform that repeats every 16 clock periods.

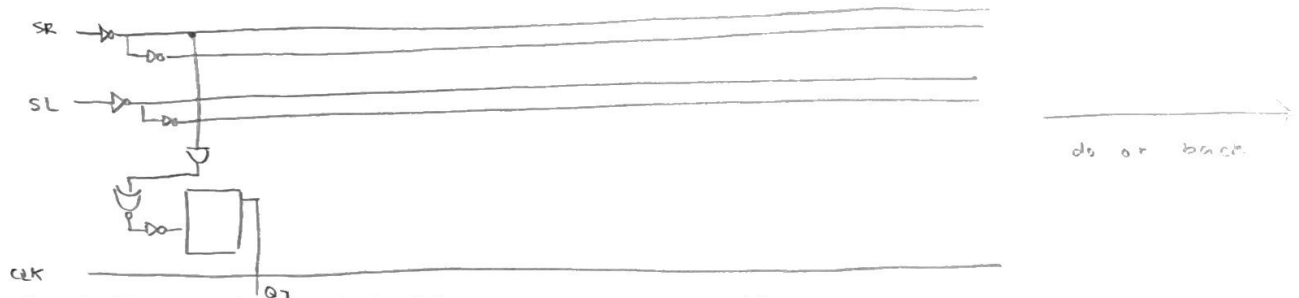

2. Consider Fig. 5, in which 4 and 5-bit Johnson counters are depicted. (a) Create a circuit based on Fig. 5 called a *combinatoric trigger*. Imagine four digital channels A, B, C, and D, as inputs. The output of the circuit should be True if *any two* of the four channels is True *within 100 ns of each other*. Develop any necessary logic symbols, and use the appropriate clock frequency. The Johnson counter(s) can have any number of bits.

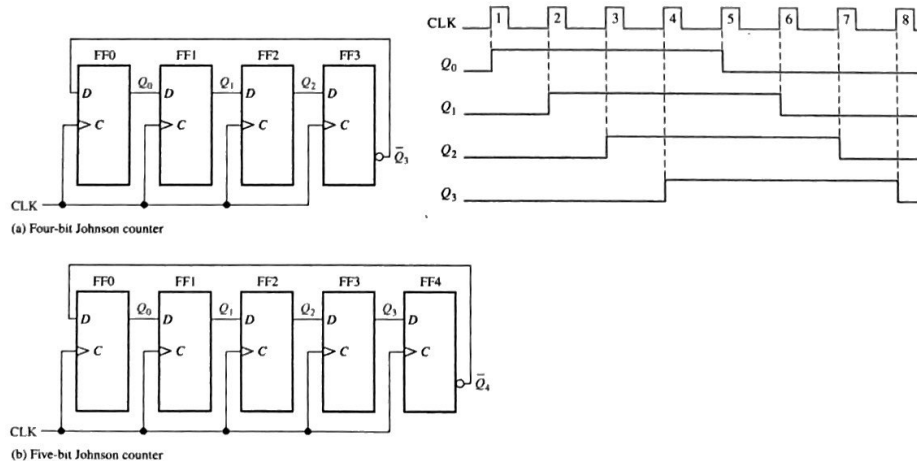


Figure 5: (Left) 4 and 5-bit Johnson counters. (Right) The timing diagram for the 4-bit case.

