

# Tuesday Reading Assessment: Chapters 6, 7

Prof. Jordan C. Hanson

March 19, 2024

## 1 Functions of Combinational Logic: Multiplexer

1. (a) Draw a diagram of the gate logic describing the 4-to-1 multiplexer, using basic AND, OR, and inverter gates. The design should include the correct number of data-select lines, four inputs, and one output. (b) Suppose that the data lines are called  $D_i$ , the data select lines are  $S_i$ , and the output line is  $D_{out}$ . If the  $S_i$  represent binary counting between 0-3, with  $1\ \mu\text{s}$  per clock step, how often can one send a bit of data to  $D_{out}$  using the  $D_0$  line? (c) How long would it take to send four bits of data, one on each  $D_i$ ?

## 2 Functions of Combinational Logic: Demultiplexer

1. (a) Draw a diagram of the gate logic describing the 1-to-4 demultiplexer, using basic AND, OR, and inverter gates. The design should include the correct number of data-select lines, one input, and four outputs. (b) Suppose that the data input line is called  $D_{in}$ , the data output lines are  $D_i$  the data select lines are  $S_i$ . The  $S_i$  represent binary counting between 0-3, with  $1\ \mu\text{s}$  per clock step. Create a timing diagram showing the behavior of  $D_{in}$ ,  $S_i$ , and  $D_i$ .