

Computer Logic and Digital Circuit Design (PHYS306/COSC330): Unit 3

Jordan Hanson

March 24, 2020

Whittier College Department of Physics and Astronomy

Summary

Unit 3 Summary

Functions of Combinatorial Logic

Reading: 6-1 - 6-6 (Tuesday)

Reading: 6-7 - 6-11 (Thursday)

1. Half-Adders and Full-Adders
 - Example from study guide
 - Propagation delays
2. Comparators
3. Decoders/Encoders

Half-Adders and Full-Adders, Ripple-Carry

Half-Adders and Full-Adders, Ripple-Carry

 


Figure 1: The desired inputs and outputs of the half-adder. There is no carry-input.

Half-Adders and Full-Adders, Ripple-Carry

TABLE 6-1

Half-adder truth table.

<i>A</i>	<i>B</i>	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Σ = sum

C_{out} = output carry

A and *B* = input variables (operands)

Figure 2: The truth table of the half-adder for 2-bits. What gate action does this match?

Half-Adders and Full-Adders, Ripple-Carry

 


Figure 3: The logic function circuit diagram for the half-adder.

Half-Adders and Full-Adders, Ripple-Carry

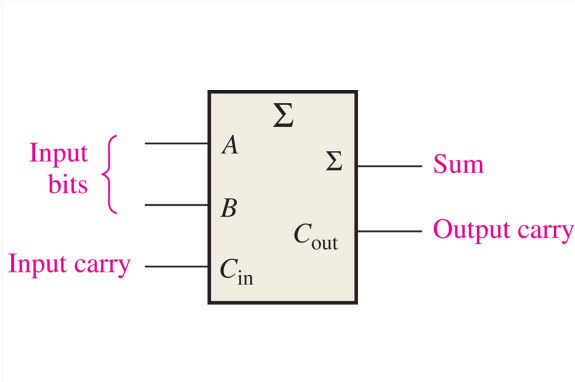


Figure 4: The desired inputs and outputs for the full-adder, with carry-input and carry-output.

Half-Adders and Full-Adders, Ripple-Carry

TABLE 6-2

Full-adder truth table.

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{in} = input carry, sometimes designated as CI


C_{out} = output carry, sometimes designated as CO

Σ = sum


A and B = input variables (operands)

Figure 5: The truth table for the full-adder is more complex due to the increased number of inputs.

 Half-Adders and Full-Adders, Ripple-Carry



 (a) Logic required to form the sum of three bits



(b) Complete logic circuit for a full-adder (each half-adder is enclosed by a shaded area)

Figure 6: Circuit diagrams for the half-adder (left) and full-adder (right).

Half-Adders and Full-Adders, Ripple-Carry

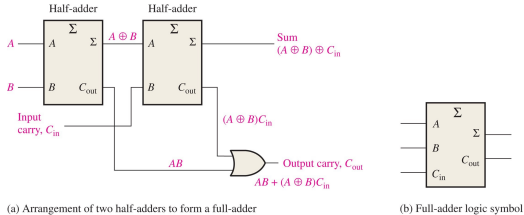


Figure 7: Two half-adders to form a full-adder.

Half-Adders and Full-Adders, Ripple-Carry

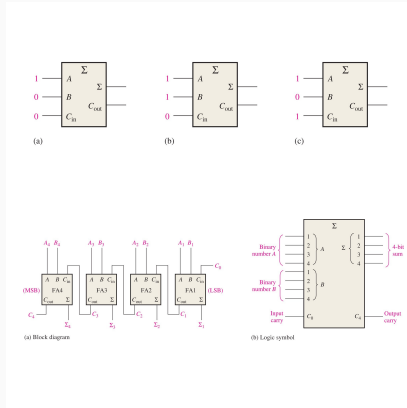


Figure 8: Four FA (full-adders) to add bits to the numbers being added.

Half-Adders and Full-Adders, Ripple-Carry

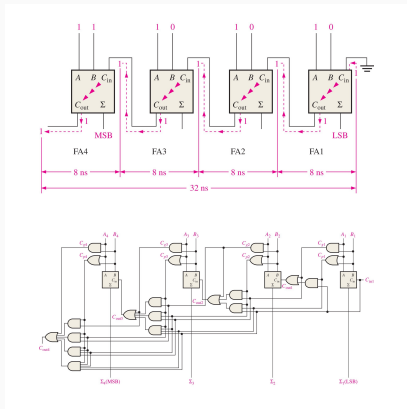


Figure 9: Propagation delays add serially in a full-adder with ripple carry topology.

Conclusion

Unit 3 Summary

Functions of Combinatorial Logic

Reading: 6-1 - 6-6 (Tuesday)

Reading: 6-7 - 6-11 (Thursday)

1. Half-Adders and Full-Adders
 - Example from study guide
 - Propagation delays
2. Comparators
3. Decoders/Encoders