

Homework 5 Solutions for Computer Logic and Circuit Design: PHYS306/COSC330

Dr. Jordan Hanson - Whittier College Dept. of Physics and Astronomy

October 25, 2021

1 6-2: Parallel Binary Adders

- Exercise 4: $C_{out} = 1$, $\Sigma_3 = 1$, $\Sigma_2 = 0$, $\Sigma_1 = 0$.
- Exercise 5: $\Sigma_6 = 1$, $\Sigma_5 = 1$, $\Sigma_4 = 1$, $\Sigma_3 = 0$, $\Sigma_2 = 0$, $\Sigma_1 = 0$.
- Exercise 8: See Fig. 1.

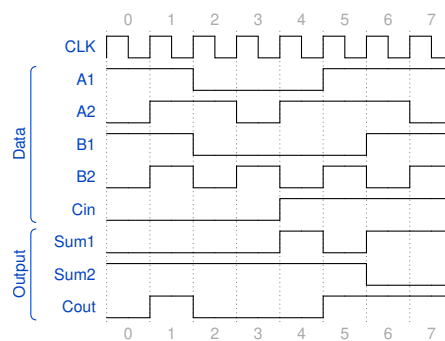


Figure 1: Solution to exercise 8.

2 6-3: Ripple-Carry Adders

- Exercise 11: The first stage is limited by 40 ns delay between inputs and C_{out} . Then, each in-between stage is limited by the 25 ns delay between C_{in} and C_{out} . The exception is the last one, which is limited only by C_{in} to Σ . Thus, $40 + 6 * 25 + 35 \text{ ns} = 225 \text{ ns}$.

3 6-4: Comparators

- Exercise 13: See Fig. 2.

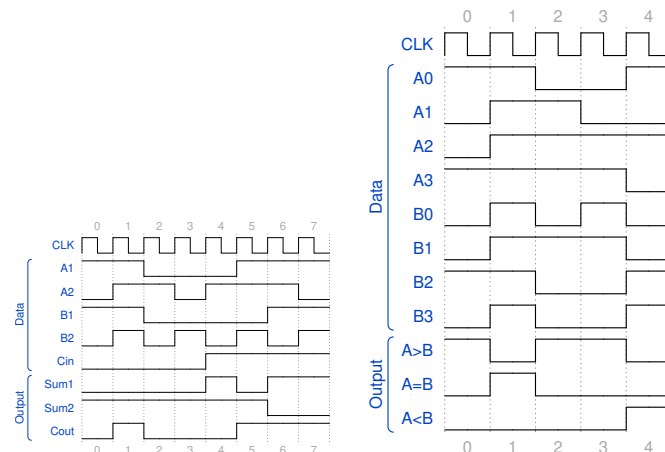


Figure 2: (Left) Solution to Exercise 13. (Right) Solution to Exercise 14.

- Exercise 14: See Fig. 2.

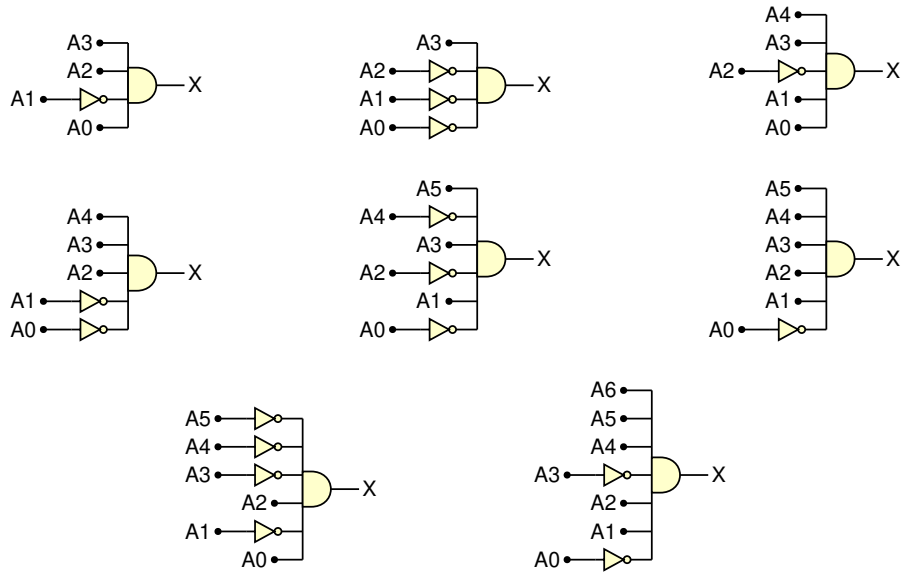


Figure 3: Solution to Exercise 17.

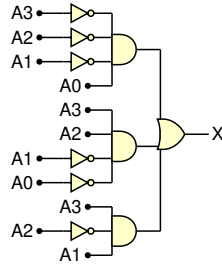


Figure 4: Solution to Exercise 19.

4 6-5: Decoders

- Exercise 16: a) 1110 b) 1100 c) 1111 d) 1000
- Exercise 17: See Fig. 3.
- Exercise 19: Using the Karnaugh map, and the starting expression $X = A_3\bar{A}_2A_1\bar{A}_0 + A_3A_2\bar{A}_1\bar{A}_0 + \bar{A}_3\bar{A}_2\bar{A}_1A_0 + A_3\bar{A}_2A_1A_0$, we can show that the minimum logic is $X = \bar{A}_3\bar{A}_2\bar{A}_1A_0 + A_3A_2\bar{A}_1\bar{A}_0 + A_3\bar{A}_2A_1$. See Fig. 4.

5 6-6: Encoders

- No, because the output would be $A_3A_2A_1A_0 = 1011$, or 11, which is not a valid BCD code.