

# COMPUTER LOGIC AND DIGITAL CIRCUIT DESIGN (PHYS306/COSC330): UNIT 2

---

Jordan Hanson

March 12, 2020

Whittier College Department of Physics and Astronomy

## SUMMARY

---

### 1. Logic Gates

- Circuit diagram
- Truth table
- Timing diagram
- Boolean logic

### 2. Boolean algebra I

### 3. Boolean algebra II

### 4. Dual logic symbols and logic diagrams

## KARNAUGH MAPS

---

A **Karnaugh Map**, or K-map, is a *cell-array*, with  $2^N$  cells, where  $N$  is the number of logical inputs.

AB \ C	0	1	AB \ C	0	1
00	000	001	00	$\bar{A} \bar{B} \bar{C}$	$\bar{A} \bar{B} C$
01	010	011	01	$\bar{A} B \bar{C}$	$\bar{A} B C$
11	110	111	11	$A B \bar{C}$	$A B C$
10	100	101	10	$A \bar{B} \bar{C}$	$A \bar{B} C$

**Table 1:** The 3-input Karnaugh map, or K-map, lists all possible outcomes of a logic operation for all possible input combinations. (Left) Bit sequence representation of all input combinations. (Right) Symbolic representation of all input combinations.

# KARNAUGH MAPS

CD \ AB	00	01	11	10
00	0000	0001	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010

CD \ AB	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$
01	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$
11	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABC\bar{D}$	$ABCD$
10	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$

**Table 2:** The 4-input K-map, in the same notation as Tab. 1.

K-maps have several requirements for *adjacent cells*.

1. **Only one bit change** between adjacent cells.
2. Cells have *wrap-around* adjacency.
3. Diagonal cells are not adjacent.

A S-SOP expression may be mapped to a K-map:

AB \ CD	00	01	11	10
00	1	1		
01		1	1	
11		1		
10		1		

**Table 3:** The 4-input K-map, with an S-SOP mapped.

S-SOP expression that is being mapped:

$$\bar{A} \bar{B} \bar{C} \bar{D} + \bar{A} \bar{B} \bar{C} D + \bar{A} B \bar{C} D + A B \bar{C} D + A \bar{B} \bar{C} D + \bar{A} B C D$$



AB \ CD	00	01	11	10
00		1		
01		1		
11		1		
10		1		

**Table 4:** The 4-input K-map, with an S-SOP mapped.

SOP expression that is being mapped:

$$\bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + AB\bar{C}D + A\bar{B}\bar{C}D$$

AB \ CD	00	01	11	10
00		1	1	
01		1	1	
11		1	1	
10		1	1	

**Table 5:** The 4-input K-map, with an S-SOP mapped.

S-SOP expression that is being mapped:

$$\bar{A} \bar{B} \bar{C} D + \bar{A} B \bar{C} D + D$$

(We must enumerate the non-standard term). We could convert to standard form, but this is faster.

S-SOP to K-map exercise:

AB \ CD	00	01	11	10
00				
01				
11				
10				

**Table 6:** Map the S-SOP expression below into the K-Map.

$$\bar{A} \bar{B} \bar{C} \bar{D} + ABC$$

S-SOP to K-map exercise:

AB \ CD	00	01	11	10
00				
01				
11				
10				

**Table 7:** Map the S-SOP expression below into the K-Map.

$$\bar{A} \bar{B} \bar{C} \bar{D} + ABCD + \bar{A} \bar{B} C D$$

## APPLIED K-MAPS: LOGIC SIMPLIFICATION

---

The expression  $\bar{A} \bar{B} \bar{C} D + \bar{A} B \bar{C} D + A B \bar{C} D + A \bar{B} \bar{C} D$  probably has a simpler form. How can we use the K-map to simplify?

---

1. *Group the 1's in adjacent cells*

- Group size must be equal to a power of 2
- Groups must be as large as possible

2. *Read simplified terms from map*

- One SOP term per group. **Exclude** contradictory variables.
- **3-variable maps:** 1-cell groups have 3-variable products, 2-cell groups with 2-variable products, 4-cell groups with 1-variable products.
- **4-variable maps:** 1-cell groups have 4-variable products, 2-cell groups with 3-variable products, 4-cell groups with 2-variable products, 8-cell groups with 1-variable products.

K-map to simplified SOP (*work several examples*):

AB \ CD	00	01	11	10
00				
01				
11				
10				

**Table 8:** Place 1's in the K-map to find the corresponding SOP expression.

K-map to simplified SOP (*use wrap-around adjacency*):

AB \ CD	00	01	11	10
00				
01				
11				
10				

**Table 9:** Place 1's in the K-map to find the corresponding SOP expression.



## APPLIED K-MAPS: LOGIC SIMPLIFICATION

Simplify:  $\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + AB\bar{C}\bar{D} + \bar{A}\bar{B}CD + A\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}BC\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D}$

AB \ CD	00	01	11	10
00				
01				
11				
10				

**Table 10:** Place 1's in the K-map to find the corresponding SOP expression. *The final expression has only two terms. Build the truth table from the final expression, and check against original expression.*

TT to minimal SOP (*work several examples*).

A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

CD \ AB	00	01	11	10
00				
01				
11				
10				

**Table 11:** The minimal SOP may be derived from a TT via the K-map.

TT to minimal SOP (utilize *don't care* conditions).


A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

CD \ AB	00	01	11	10
00				
01				
11				
10				

**Table 12:** The minimal SOP may be derived from a TT via the K-map.

# COMBINATORIAL LOGIC AND DUAL LOGIC SYMBOLS

---

 

**Figure 1:** An example of a combinatorial logic circuit involving inverters. What if we arranged the circuit without single inverters?

*Hint: move the last bubble backwards one step.*

# COMBINATORIAL LOGIC AND DUAL LOGIC SYMBOLS



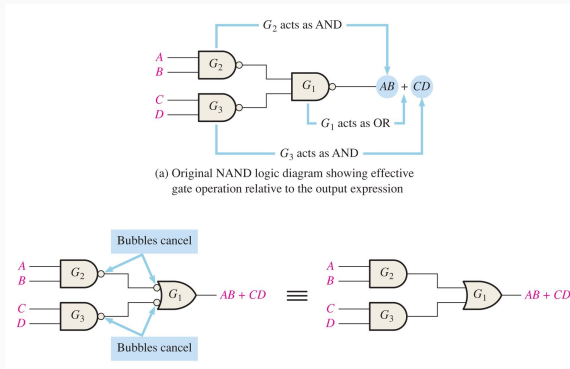


Figure 2: The solution to Fig. 1.
 
# COMBINATORIAL LOGIC AND DUAL LOGIC SYMBOLS



 (a) Several Boolean steps are required to arrive at final output expression.



(b) Output expression can be obtained directly from the function of each gate symbol in the diagram.

**Figure 3:** Notice how the active LOW states mid-circuit are simplifying the interpretation of the circuit.

 


Figure 4: Solve for X.



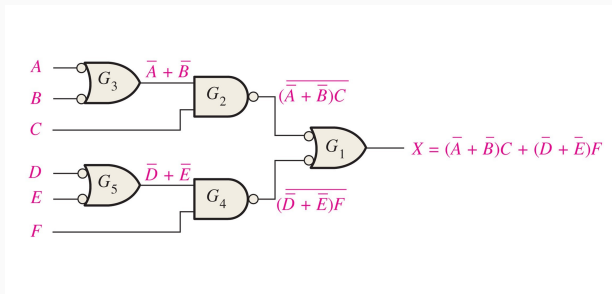


Figure 5: Answer for Fig. 4.

## CONCLUSION

---

### 1. Logic Gates

- Circuit diagram
- Truth table
- Timing diagram
- Boolean logic

### 2. Boolean algebra I

### 3. Boolean algebra II

### 4. Dual logic symbols and logic diagrams