

Computer Logic and Digital Circuit Design (PHYS306/COSC330): Unit 1

Jordan Hanson

September 28, 2021

Whittier College Department of Physics and Astronomy

Summary

Unit 1 Summary - Theoretical Logic Gates, and Operations

1. Logic Gates
 - Circuit diagram
 - Truth table
 - Timing diagram
 - Boolean logic
2. Boolean algebra I
3. Boolean algebra II
4. Dual logic symbols and logic diagrams

Karnaugh Maps

Karnaugh Maps

A **Karnaugh Map**, or K-map, is a *cell-array*, with 2^N cells, where N is the number of logical inputs.

<div>AB \ C</div>	0	1	<div>AB \ C</div>	0	1
00	000	001	00	$\overline{A} \overline{B} \overline{C}$	$\overline{A} \overline{B} C$
01	010	011	01	$\overline{A} B \overline{C}$	$\overline{A} B C$
11	110	111	11	$A B \overline{C}$	$A B C$
10	100	101	10	$A \overline{B} \overline{C}$	$A \overline{B} C$

Table 1: The 3-input Karnaugh map, or K-map, lists all possible outcomes of a logic operation for all possible input combinations. (Left) Bit sequence representation of all input combinations. (Right) Symbolic representation of all input combinations.

Karnaugh Maps

AB \ CD	00	01	11	10
00	0000	0001	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010

AB \ CD	00	01	11	10
00	$\bar{A} \bar{B} \bar{C} \bar{D}$	$\bar{A} \bar{B} \bar{C} D$	$\bar{A} \bar{B} C D$	$\bar{A} \bar{B} C \bar{D}$
01	$\bar{A} B \bar{C} \bar{D}$	$\bar{A} B \bar{C} D$	$\bar{A} B C D$	$\bar{A} B C \bar{D}$
11	$A B \bar{C} \bar{D}$	$A B \bar{C} D$	$A B C D$	$A B C \bar{D}$
10	$A \bar{B} \bar{C} \bar{D}$	$A \bar{B} \bar{C} D$	$A \bar{B} C D$	$A \bar{B} C \bar{D}$

Table 2: The 4-input K-map, in the same notation as Tab. 1.

Karnaugh Maps

K-maps have several requirements for *adjacent cells*.

1. **Only one bit change** between adjacent cells.
2. Cells have *wrap-around* adjacency.
3. Diagonal cells are not adjacent.

Karnagh Maps: Mapping S-SOP expressions

A S-SOP expression may be mapped to a K-map:

AB \ CD	00	01	11	10
00	1	1		
01		1	1	
11		1		
10		1		

Table 3: The 4-input K-map, with an S-SOP mapped.

S-SOP expression that is being mapped:

$$\overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} \overline{C} D + \overline{A} B \overline{C} D + A B \overline{C} D + A \overline{B} \overline{C} D + \overline{A} B C D$$

Karnagh Maps: Mapping S-SOP expressions

AB \ CD	00	01	11	10
00		1		
01		1		
11		1		
10		1		

Table 4: The 4-input K-map, with an S-SOP mapped.

SOP expression that is being mapped:

$$\overline{A} \overline{B} \overline{C} D + \overline{A} B \overline{C} D + A B \overline{C} D + A \overline{B} \overline{C} D$$

Karnagh Maps: Mapping non-standard SOP expressions

CD \ AB	00	01	11	10
00		1	1	
01		1	1	
11		1	1	
10		1	1	

Table 5: The 4-input K-map, with an S-SOP mapped.

S-SOP expression that is being mapped:

$$\overline{A} \overline{B} \overline{C} D + \overline{A} B \overline{C} D + D$$

(We must enumerate the non-standard term). We could convert to standard form, but this is faster.

Karnagh Maps: Mapping S-SOP expressions

S-SOP to K-map exercise:

AB \ CD	00	01	11	10
00				
01				
11				
10				

Table 6: Map the S-SOP expression below into the K-Map.

$$\overline{A} \overline{B} \overline{C} \overline{D} + ABC$$

Karnagh Maps: Mapping S-SOP expressions

S-SOP to K-map exercise:

AB \ CD	00	01	11	10
00				
01				
11				
10				

Table 7: Map the S-SOP expression below into the K-Map.

$$\overline{A} \overline{B} \overline{C} \overline{D} + ABCD + \overline{A} \overline{B} C D$$

Applied K-Maps: Logic Simplification

Applied K-Maps: Logic Simplification

The expression $\bar{A} \bar{B} \bar{C} D + \bar{A} B \bar{C} D + A B \bar{C} D + A \bar{B} \bar{C} D$ probably has a simpler form. How can we use the K-map to simplify?

1. *Group the 1's in adjacent cells*

- Group size must be equal to a power of 2
- Groups must be as large as possible

2. *Read simplified terms from map*

- One SOP term per group. **Exclude** contradictory variables.
- **3-variable maps:** 1-cell groups have 3-variable products, 2-cell groups with 2-variable products, 4-cell groups with 1-variable products.
- **4-variable maps:** 1-cell groups have 4-variable products, 2-cell groups with 3-variable products, 4-cell groups with 2-variable products, 8-cell groups with 1-variable products.

Applied K-Maps: Logic Simplification

K-map to simplified SOP (*work several examples*):

AB \ CD	00	01	11	10
00				
01				
11				
10				

Table 8: Place 1's in the K-map to find the corresponding SOP expression.

Applied K-Maps: Logic Simplification

K-map to simplified SOP (*use wrap-around adjacency*):

AB \ CD	00	01	11	10
00				
01				
11				
10				

Table 9: Place 1's in the K-map to find the corresponding SOP expression.

Applied K-Maps: Logic Simplification

Simplify: $\overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + \overline{A} \overline{B} C D + A \overline{B} C D + \overline{A} \overline{B} C \overline{D} + \overline{A} B C \overline{D} + A B C \overline{D} + A \overline{B} C \overline{D}$

AB \ CD	00	01	11	10
00				
01				
11				
10				

Table 10: Place 1's in the K-map to find the corresponding SOP expression. *The final expression has only two terms. Build the truth table from the final expression, and check against original expression.*

Applied K-Maps: Logic Simplification

TT to minimal SOP (*work several examples*).

A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

AB \ CD	00	01	11	10
00				
01				
11				
10				

Table 11: The minimal SOP may be derived from a TT via the K-map.

Applied K-Maps: Logic Simplification

TT to minimal SOP (*utilize **don't care** conditions*).

A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

AB \ CD	00	01	11	10
00				
01				
11				
10				

Table 12: The minimal SOP may be derived from a TT via the K-map.

Combinatorial Logic and Dual Logic Symbols

Combinatorial Logic and Dual Logic Symbols

 


Figure 1: An example of a combinatorial logic circuit involving inverters. What if we arranged the circuit without single inverters?

Hint: move the last bubble backwards one step.

Combinatorial Logic and Dual Logic Symbols

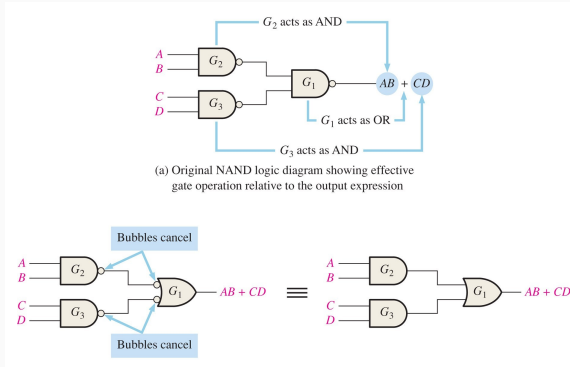


Figure 2: The solution to Fig. 1.

Combinatorial Logic and Dual Logic Symbols

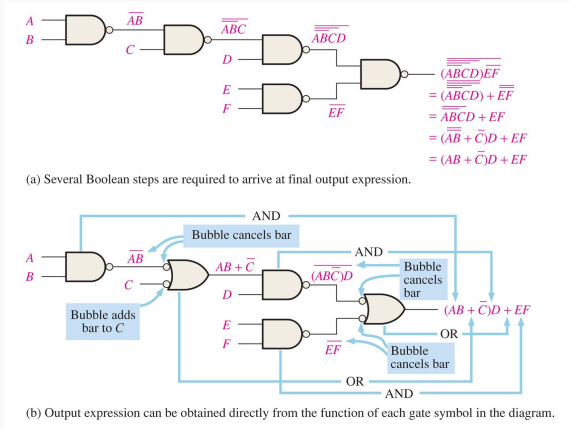


Figure 3: Notice how the active LOW states mid-circuit are simplifying the interpretation of the circuit.

Combinatorial Logic and Dual Logic Symbols

 


Figure 4: Solve for X .

Combinatorial Logic and Dual Logic Symbols

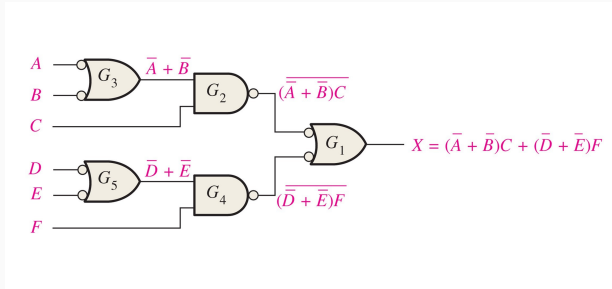


Figure 5: Answer for Fig. 4.

Conclusion

Unit 1 Summary - Theoretical Logic Gates, and Operations

1. Logic Gates
 - Circuit diagram
 - Truth table
 - Timing diagram
 - Boolean logic
2. Boolean algebra I
3. Boolean algebra II
4. Dual logic symbols and logic diagrams