

Synopsis - Week 7 Integrated Project: fixed IC gates and counters, gates and counters in programmable logic

Prof. Jordan C. Hanson

October 13, 2023

1 Finite Impulse Response (FIR) Filter

A finite impulse response (FIR) filter takes digitized data as the input, and returns modified data of the same shape as the output. Let n represent the number of samples of digitized data. Let $x[n]$ represent the vector of digitized input data, and $y[n]$ represent the digitized output data. Let z^{-1} represent an operation that selects the prior sample, or the $n - 1$ sample relative to sample n . Let the coefficients b_n multiply the samples $x[n]$ as they pass through an amplifier. Finally, let Σ represent an adder that sums to inputs and produces one output. A generalized circuit diagram for the FIR filter is shown in Fig. 1, and the formula relating the input to the output is given in Eq. ??.

 


Figure 1: A generalized circuit diagram for the FIR filter.

$$y[n] = \sum_{i=0}^N b_i x[n - i] \quad (1)$$

In this lab, we are going to create a PYNQ overlay that will implement Eq. 1 in the SoC PL layer.

2 Comparing fixed IC gates and counters to programmable logic

1. Things