

# Computer Logic and Digital Circuit Design (PHYS306/COSC330): Unit 3

---

Jordan Hanson

March 21, 2024

Whittier College Department of Physics and Astronomy

## Summary

---

# Unit 3 Summary

## Reading: chapter 7


We now know how to generate and process digital data. We can do algebra, compare numbers, encode, decode, and multiplex. *How does memory work? How is information held in digital systems?*

1. S-R latches
  - Basic latch, de-bounce
  - Gated latch
  - D-latch
2. Flip-flops
  - JK flip-flops
  - Synchronous vs. level-sensitive
3. Flip-flop applications

# S-R Latches

---

# S-R Latches

 

(a) Active-HIGH input S-R latch (b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch

 


TABLE 7-1

Truth table for an active-LOW input  $\bar{S}$ - $\bar{R}$  latch.

Inputs		Outputs		Comments
$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$	
1	1	NC	NC	No change. Latch remains in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition

**Figure 1:** An S-R latch is a *multivibrator* that holds its state when SET, or RESET.

# S-R Latches


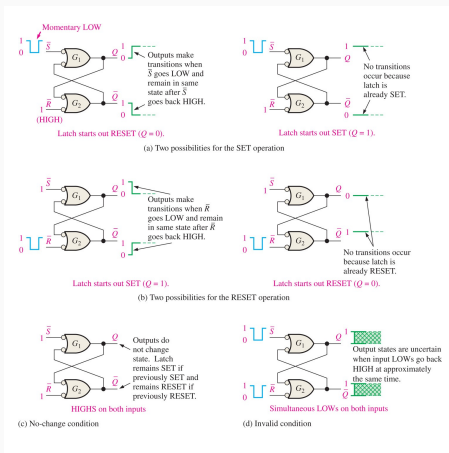



Figure 2: Summary of potential states of a basic S-R latch.

# S-R Latches

 

**Figure 3:** The basic, gate-enabled, and D-latch systems. For the latter two, both the gate and symbol are shown.

# S-R Latches

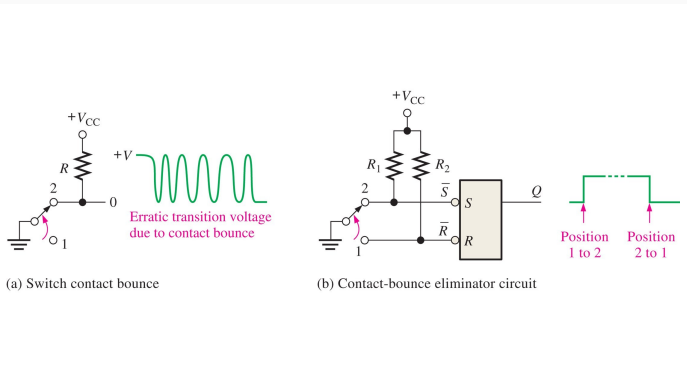

**Figure 4:** De-bouncing is important any time a mechanical switch is meant to interact with digital logic.



# Flip Flops

---

# Flip-Flops


 


Figure 5: Four types of **synchronous** latches called flip-flops.

# Flip-Flops

 

**TABLE 7-2**

Truth table for a positive edge-triggered D flip-flop.

Inputs		Outputs		Comments
$D$	CLK	$Q$	$\overline{Q}$	
0	↑	0	1	RESET
1	↑	1	0	SET

↑ = clock transition LOW to HIGH

**Figure 6:** The symbol and TT for the D-flip flop. The behavior is similar to a D-latch without enable, but only on positive edge of clock (posedge).

# Flip-Flops


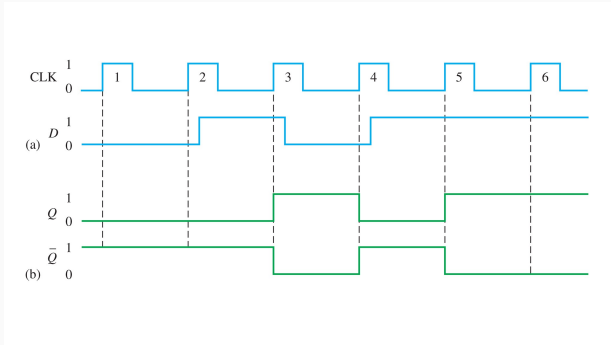


Figure 7: Example of D flip-flop behavior.

# Flip-Flops

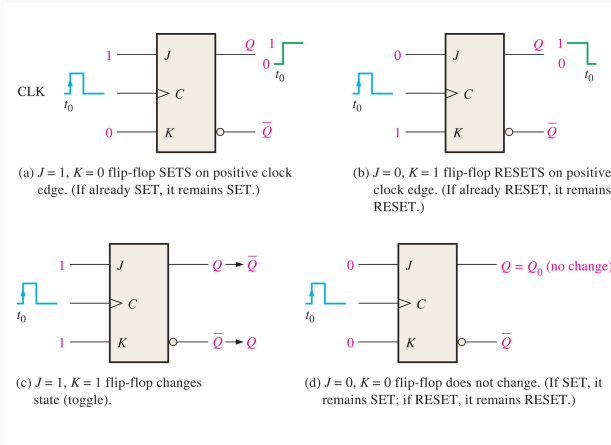

**Figure 8:** The JK flip flop, triggered on posedge. There are still the SET and RESET states, but the other two states differ from the SR latch.

# Flip-Flops



**TABLE 7-3**

Truth table for a positive edge-triggered J-K flip-flop.

Inputs			Outputs		Comments
$J$	$K$	CLK	$Q$	$\bar{Q}$	
0	0	↑	$Q_0$	$\bar{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\bar{Q}_0$	$Q_0$	Toggle


↑ = clock transition LOW to HIGH

$Q_0$  = output level prior to clock transition

  


**Figure 9:** The TT for the JK flip flop, which is also **synchronous**. An example timing diagram is given for the JK as well.

# Flip-Flops

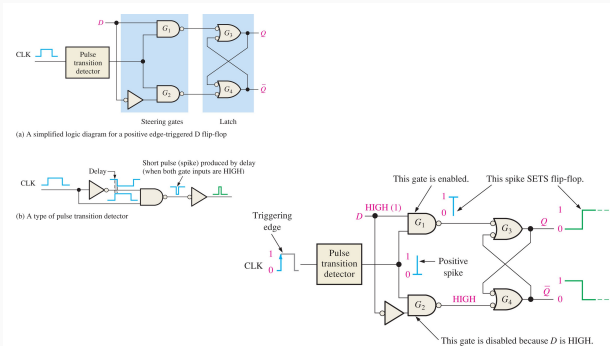

**Figure 10:** How does the posedge triggering work? Physically, it is based on *propagation delay*. The D flip-flop is pictured as an example, with spikes. *What counts as a spike?*


# Flip-Flops

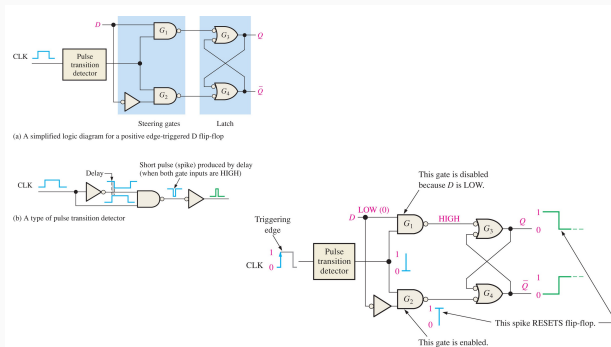

**Figure 11:** How does the posedge triggering work? Physically, it is based on *propagation delay*. The D flip-flop is pictured as an example, with spikes. *What counts as a spike?*




# Flip-Flops

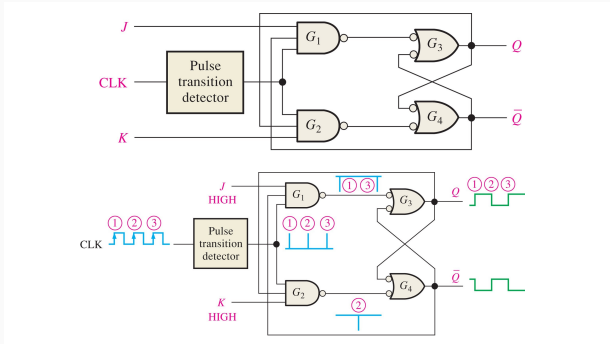



**Figure 12:** Circuit diagram with symbols for the JK flip flop, with posedge trigger. The JK flip-flop is in **toggle** mode.

# Flip-Flops

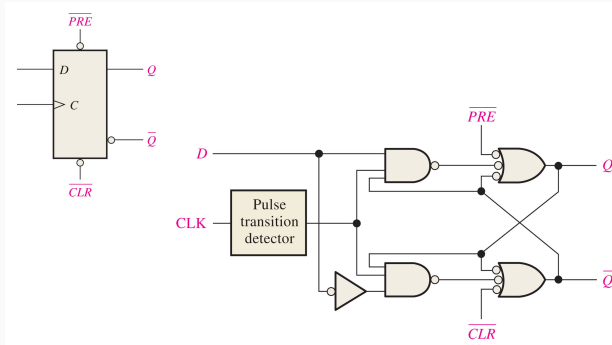

**Figure 13:** Add two asynchronous features, preset and clear. These override the synchronous features due to the way they are used.

# Flip-Flops

  

# Flip Flop Applications

---

# Flip Flop Applications

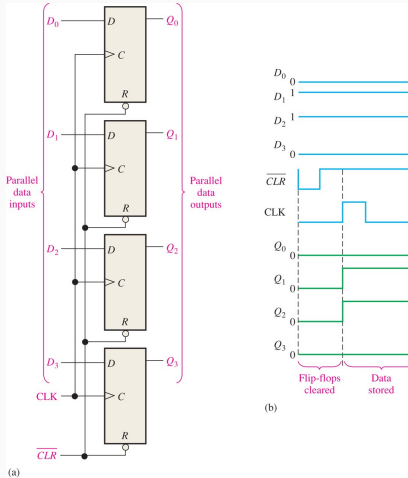


Figure 15: 4-bit parallel memory storage.

# Flip Flop Applications

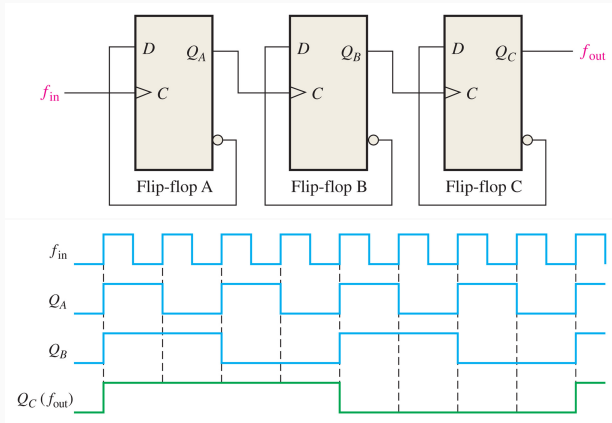


Figure 16: Frequency divider. What is the ratio  $f_{out}/f_{in}$ ?

# Flip Flop Applications

 


Figure 17: A 3-bit counter built from 3 JK flip-flops.

# Conclusion

---



# Unit 3 Summary

## Reading: chapter 7

We now know how to generate and process digital data. We can do algebra, compare numbers, encode, decode, and multiplex. *How does memory work? How is information held in digital systems?*

1. S-R latches
  - Basic latch, de-bounce
  - Gated latch
  - D-latch
2. Flip-flops
  - JK flip-flops
  - Synchronous vs. level-sensitive
3. Flip-flop applications

*Move the subject of timers to later date.*