

Simplified circuit for an OR gate

$X = A + B + C + D$

Figure 2: Example circuit for chapter 5.

Chapter 4 - Boolean Algebra and Logic Simplification

1. Map the expression $X = A + CD + ACD + ABCD$ onto a Karnaugh map, group the true states, and develop the simplified logic expression for the output X .

00	01	11	10
00	1	1	1
01		1	1
11		1	1
10		1	1

$$\begin{aligned}
 & \overline{A}\overline{B} + \overline{A}B + A\overline{B} + AB \\
 & (\overline{A}(\overline{B} + B) + A(\overline{B} + B)) + \overline{C}DB \\
 & (\overline{A} + A) + \overline{C}DB + \overline{C}DBA + \overline{C}DBA \\
 & \overline{C}DB + \overline{C}DB(A + A)
 \end{aligned}$$



Chapter 5 - Combinational Logic Analysis

1. In Fig. 2, a logic function is shown that outputs 1 if exactly three inputs are 1. (a) Develop the truth table (true states only). (b) Determine if it can be simplified.

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Chapter 6 - Functions of Combinational Logic

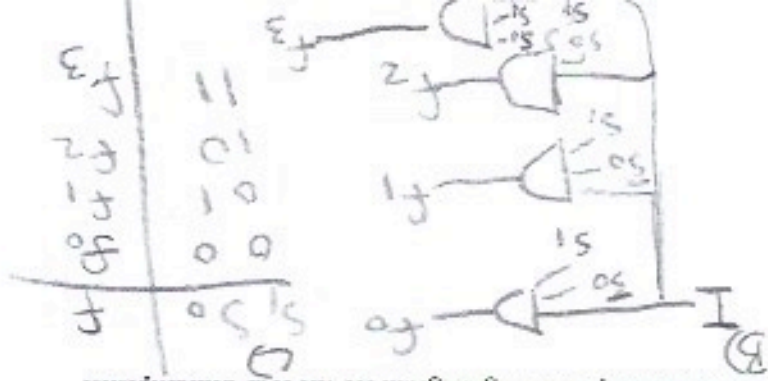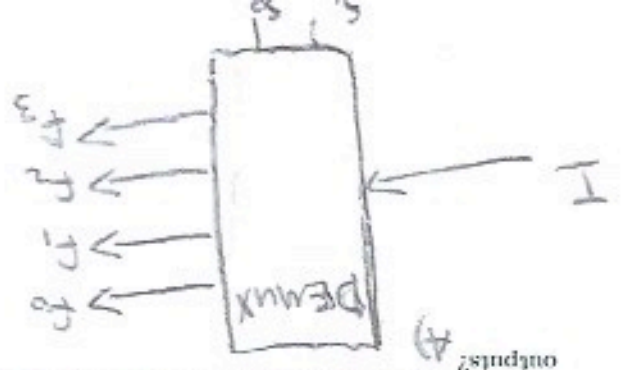1. Suppose you have a counter that accepts a clock signal as input, and has two outputs that cycle between 00, 01, 10, and 11. (a) Draw a circuit connecting the 2-bit counter to the data select lines of a 1-to-4 demultiplexer. (b) Now connect also the counter output to a 2-bit parity checker (XOR gate), and let the output of the parity checker be the data input to the demultiplexer. (c) What is the output timing diagram for the four demultiplexer outputs?



f3	11	01	00	00
f2	10	01	00	00
f1	01	01	00	00
f0	00	01	00	00


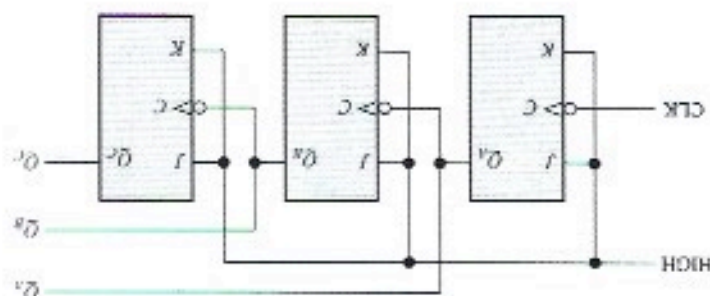


Figure 3: Example circuit for chapter 7.


7 Chapter 7 - Latches, Flip-flops, and Timers

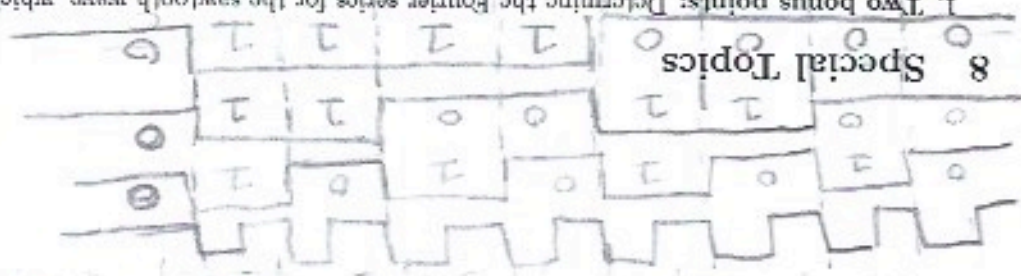- Remember the counter mentioned in the previous problem? Consider Fig. 3. Determine the output waveforms in relation to the clock for Q_A , Q_B , and Q_C , and show that $Q_C Q_B Q_A$ is the binary sequence 000, 001, 010, 011, 100, 101, 110, and 111. The outputs go through the binary sequence



8 Special Topics

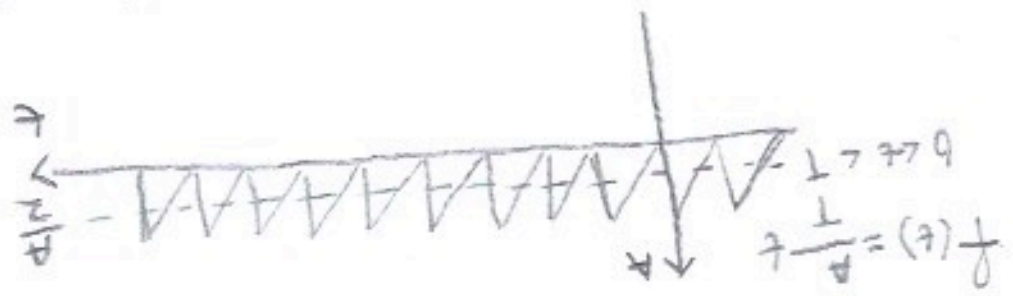- Two bonus points: Determine the Fourier series for the sawtooth wave, which is just $f(x) = x$ from 0 to 2π , after which it goes back to zero and repeats itself.



$$f(\omega) = \frac{1}{T} \omega = 2\pi f = \frac{2\pi}{T}$$

If a repeats itself then the Fourier series of this function is $\int_{-\infty}^{\infty}$

$$f(x) = a_0 + \sum_{n=1}^{\infty} [a_n \cos nx + b_n \sin nx]$$

#4

$$\begin{aligned} & ABCD + ABC\bar{D} + AB\bar{C}D + A\bar{B}CD + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + \\ & A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \\ & \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} \end{aligned}$$