

Thursday Reading Assessment: ADC and DAC (Chapter 12 + Lab)

Prof. Jordan C. Hanson

April 4, 2024

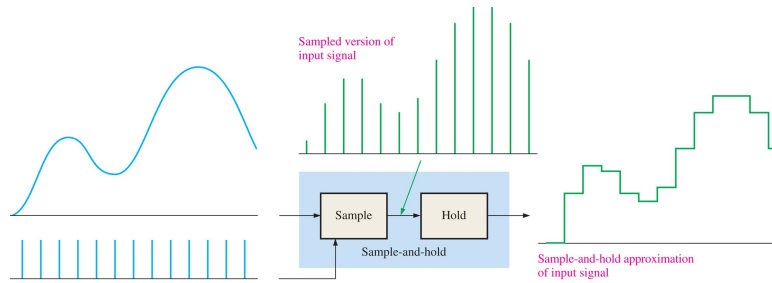


Figure 1: Simple picture of the sample-and-hold step in analog-to-digital conversion.

1 Analog-to-Digital Conversion

1. **Analog-to-digital conversion** (ADC) is a 2-step process by which analog signals are converted to digital data in digital circuits. The first step is depicted in Fig. 1 (top left, top right). In a **sample-and-hold** operation, the continuous signal is mixed with *sample pulses* emitted at rate equal to the sampling frequency. (Fig. 1 (top left)). The mixed sample pulses then cause a latch to *hold* the voltage value for the duration of the sample, $\Delta t = f_s^{-1}$ (Fig. 1 (top right)). (a) If Δt is $1 \mu s$, what is the sampling frequency? (b) What is the Nyquist frequency?
2. In the next stage of ADC, the sample-and-hold output is *digitized*. Assume the space between maximum voltage, V_{CC} , and $0V$, is quantized with N bits. (a) If $V_{CC} = 5.0 V$, and $N = 3$ bits, what is the voltage resolution? (b) If $V_{CC} = 12.0 V$, and $N = 12$ bits, what is the voltage resolution? (c) If we need at least $10 mV$ precision for $V_{CC} = 5.0 V$, what is the minimum number of ADC bits?

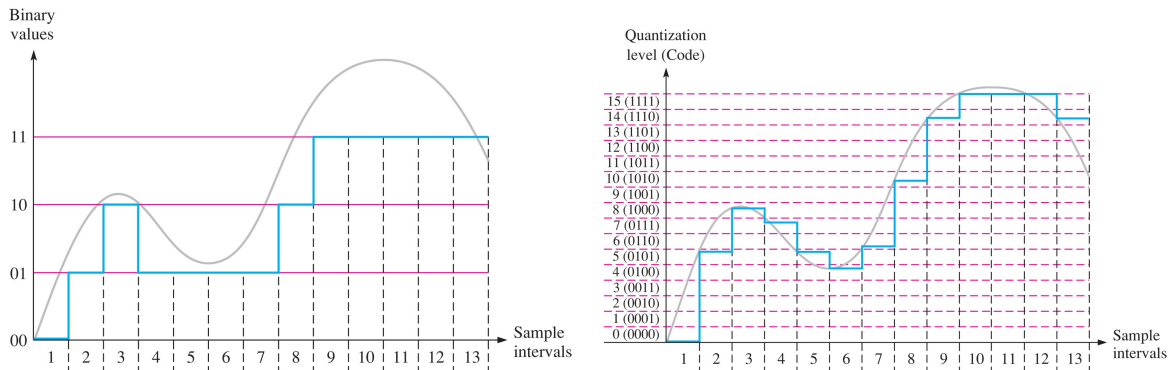


Figure 2: (Left) 2-bit ADC precision. (Right) 4-bit ADC precision.

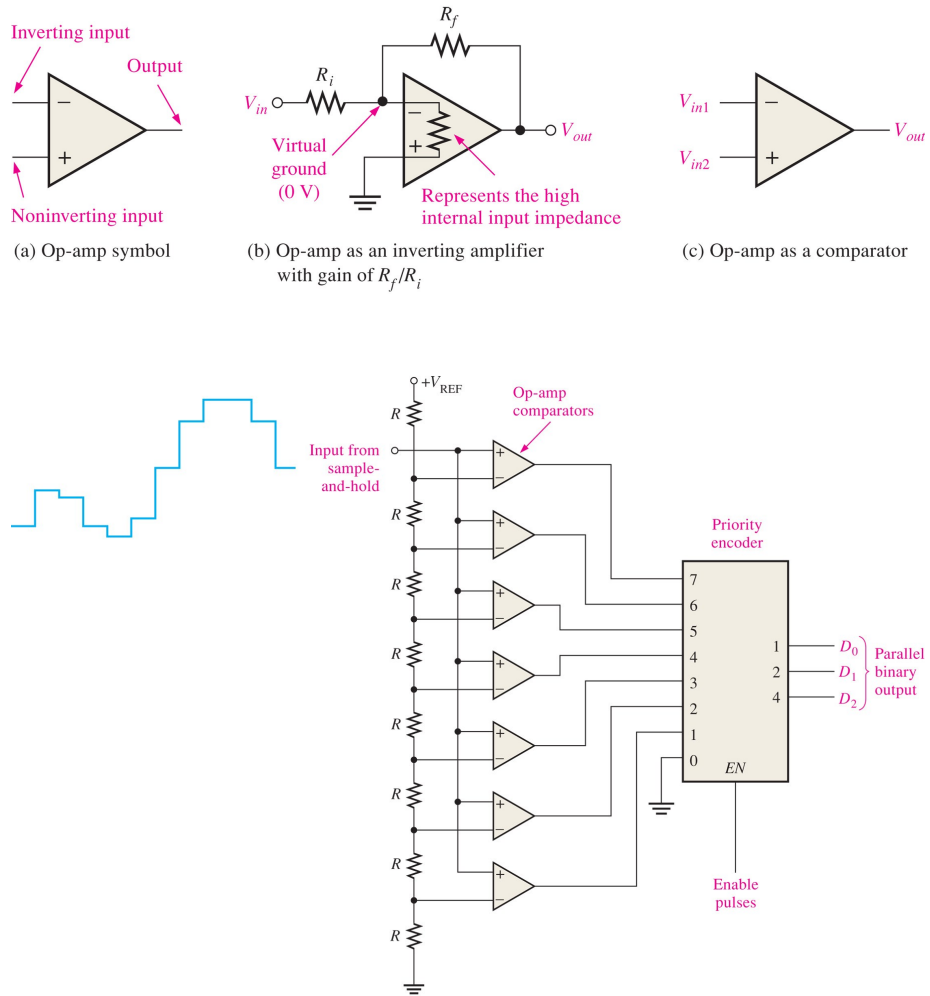


Figure 3: (Top) Op-amp characteristics. (Bottom) 3-bit flash ADC schematic.