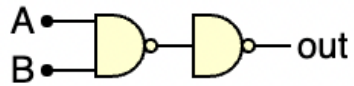



1. AND gate made from NANDs

```
{ assign:[  
  ["out",  
    ["~&", ["~&", "A", "B"]  
  ]  
]  
}]
```



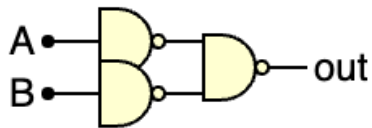2. OR gate made from NANDs

```
{ assign:[  
  ["out",  
    ["~&",  
      ["~&", "A", ],  
      ["~&", "B", ]  
    ]  
]  
}]
```



3. XOR gate made from NANDs

```
{ assign:[  
  ["out",  
    ["~&",  
      ["~&", "A",  
        ["~&", "A", "B", ],  
        ["~&", "B",  
          ["~&", "A", "B", ]  
        ]  
      ]  
    ]  
]  
}]
```

